

EN1020 Circuits, Signals and Systems

Topic 05 - Two-Port Networks

Upeka Premaratne

Department of Electronic and Telecommunication Engineering

July, 2022


Outline

- 1 Introduction
- 2 System Transfer Operations
- 3 Two-Port Networks
 - Impedance Parameters
 - Admittance Parameters
 - Hybrid Parameters
 - ABCD Parameters
- 4 Matrix Estimation
- 5 Conclusion

Introduction


Introduction

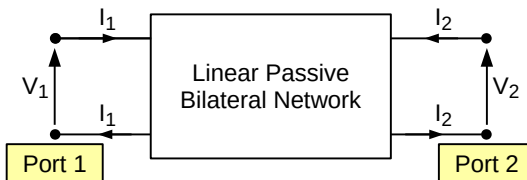- Two-port networks is a method of describing the behavior of linear passive bilateral circuit with two port connections in terms of parameters obtained from measurements
 - ▶ Makes it unnecessary to thoroughly analyze the circuit



Black Box Approach

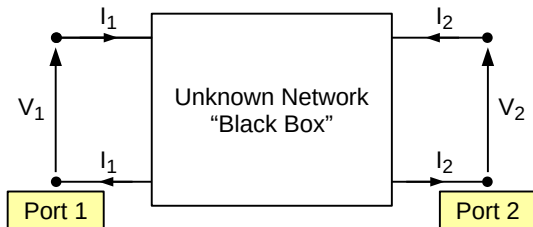- A further advantage of using two-port networks is that it can be used to approximate an unknown circuit based entirely on measurements
- These parameters can then be used to calculate a multitude of important system parameters related to transfer operations




System Transfer Operations

System Transfer Operations


- A transfer operation from the input to the output is often the main requirement of an electrical or electronic circuit
- For example
 - ▶ A passive filter (voltage transfer)
 - ▶ A pre-amplifier (voltage transfer)
 - ▶ A power amplifier (power transfer through current transfer)
- Therefore, realization of or analysis of a circuit to improve a transfer operation is a common design requirement
 - ▶ Two-port networks provide a convenient description for this purpose for most passive and small signal active networks

Source and Load Connection Model

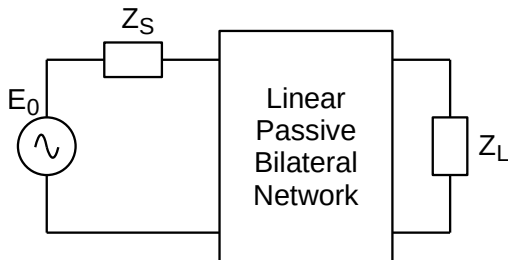- The objective is to commonly maximize delivery of
 - 1 The input to the system
 - 2 The system output to the load
- Applicable to active networks as well



Voltage Transfer

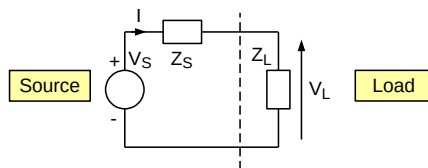


- Voltage transfer to the load

$$V_L = \frac{Z_L V_S}{Z_L + Z_S}$$

- To maximize voltage transfer ($V_L \rightarrow V_S$)
 - Typically requires $|Z_L| \gg |Z_S|$

Current Transfer

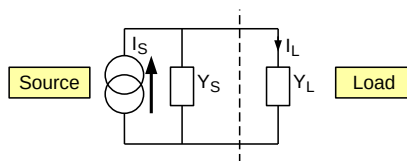


- Current transfer to the load

$$I_L = \frac{Y_L I_S}{Y_L + Y_S}$$

- To maximize current transfer ($I_L \rightarrow I_S$)
 - ▶ Requires $|Y_L| \gg |Y_S|$
 - ▶ In most cases unrealistic

Power Transfer

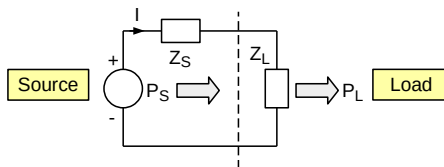

- Power from the source is delivered to the load
- Since $P = VI$ different from current or voltage transfer
- Two cases have to be considered
 - 1 Resistive load (no reactance)
 - 2 Complex load (resistive and reactive)

Resistive Load

$$I = \frac{V_S}{R_S + R_L}$$

$$P_L = V_L I = \left(\frac{R_L V_S}{R_S + R_L} \right) \left(\frac{V_S}{R_S + R_L} \right)$$

$$= \frac{R_L V_S^2}{(R_S + R_L)^2}$$

$$\frac{d}{dR_L} P_L = \frac{V_S^2}{(R_S + R_L)^4} [(R_S + R_L)^2 - 2R_L(R_S + R_L)] = 0$$

$$\Rightarrow R_S = R_L \text{ (For maximum power transfer)}$$

Complex Load

- Take $Z_S = R_S + jX_S$ and $Z_L = R_L + jX_L$

$$I = \frac{V_S}{(R_S + R_L) + j(X_S + X_L)}$$

$$P_L = |I|^2 R_L = \frac{V_S^2 R_L}{\sqrt{(R_S + R_L)^2 + (X_S + X_L)^2}}$$

- To find the maximum dissipated P_L has to be differentiated w.r.t. both R_L and X_L

$$\frac{\partial}{\partial R_L} P_L = \frac{V_S^2 \left[[(R_S + R_L)^2 + (X_S + X_L)^2] - 2R_L(R_S + R_L) \right]}{[(R_S + R_L)^2 + (X_S + X_L)^2]^2}$$

Complex Load (Contd..)

$$\frac{\partial}{\partial X_L} P_L = - \frac{V_S^2 [-2R_L(X_S + X_L)]}{[(R_S + R_L)^2 + (X_S + X_L)^2]^2}$$

- $\frac{\partial}{\partial X_L} P_L = 0$ results in $X_S = -X_L$
- $X_S = -X_L$ with $\frac{\partial}{\partial R_L} P_L = 0$ results in $R_S = R_L$
- Therefore, $Z_S = Z_L^*$ for maximum power transfer

Power Transfer Efficiency

- Maximum power transfer gives the maximum power that can be *extracted* from the load
- The power efficiency is given by


$$\eta = \frac{P_L}{P_S} = \frac{V_L I}{V_S I} = \frac{R_L}{(R_L + R_S)}$$

- At maximum power transfer the system is only 50% efficient
 - ▶ Half the power is lost in the source as heat
- For maximum power transfer efficiency $R_S \ll R_L$
 - ▶ Same conditions for maximizing voltage transfer
 - ▶ However, there are often practical limitations

Power Transfer Efficiency (Contd..)

- The importance of maximum power transfer and high power transfer efficiency depend on the application
 - ▶ Driving a motor or a power supply will require maximum power transfer efficiency to minimize power wastage
 - ▶ A sensitive sensor that provides a small power output may require maximum power to be extracted for the best result
 - ▶ Audio power amplifiers seek to maximize power output (that is why speaker impedances have to be matched)

Terminated Two-Port Network Model

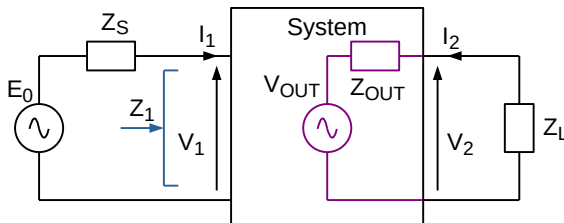

- Port 1 is taken as the input and Port 2 is taken as the output
- The source impedance and input impedance $z_{IN} = z_1$ forms a potential divider for the source
- The output impedance Z_{OUT} forms a Thevenin impedance with the output “source” V_{OUT}

Impedance Parameters

- Impedance parameters are obtained as ratios when one port is open circuited (i.e., $I_1 = 0$ or $I_2 = 0$)
- Feed impedance parameters

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

- ▶ z_{11} is the feed impedance of Port 1 when Port 2 is OC
- ▶ z_{22} is the feed impedance of Port 2 when Port 1 is OC
- ▶ If the network is symmetric $z_{11} = z_{22}$

Impedance Parameters

Impedance Parameters (Contd..)

■ Trans-impedance parameters

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

- ▶ z_{12} is the TI of the OC voltage of Port 1 and current of Port 2
- ▶ z_{21} is the TI of the OC voltage of Port 2 and current of Port 1
- ▶ If the network is reciprocal $z_{12} = z_{21}$

- $$\begin{pmatrix} V_1 \\ V_2 \end{pmatrix} = \begin{pmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix}$$

-
- The diagram shows a two-port network. The left port has an input voltage V_1 and current I_1 entering a rectangular block labeled z_{11} . The right port has an input voltage V_2 and current I_2 entering a rectangular block labeled z_{22} . A dependent voltage source, represented by a diamond with a '+' sign at the top and a '-' sign at the bottom, is connected between the output of the z_{11} block and the common ground. This source is labeled $z_{12}I_2$. Another dependent voltage source, also a diamond with '+' and '-' signs, is connected between the output of the z_{22} block and the common ground. This source is labeled $z_{21}I_1$. All components are connected to a common ground line at the bottom.

Impedance Parameters (Contd..)

- For a terminated network

$$z_{IN} = z_{11} - \left(\frac{z_{12}z_{21}}{z_{22} + z_L} \right)$$


$$z_{OUT} = z_{22} - \left(\frac{z_{12}z_{21}}{z_{11} + z_S} \right)$$

$$A_I = \frac{I_2}{I_1} = \frac{-z_{21}}{z_{22} + z_L}$$

$$A_V = \frac{V_2}{V_1} = \frac{z_{21}z_L}{z_{11}z_L + |Z|}$$

$$A_S = \frac{V_2}{V_S} = \frac{z_{21}z_L}{(z_{11} + z_S)(z_{22} + z_L) - z_{12}z_{21}}$$

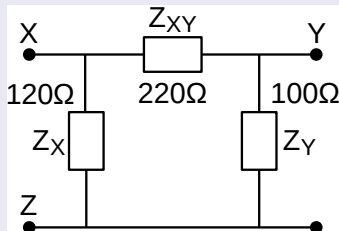- 1 Find the impedance parameter matrix of the following network
- 2 What will be the overall gain when the network is terminated with a load of $100\ \Omega$ and connected to a source with an impedance of $10\ \Omega$?



Impedance Parameters (Contd..)

- Impedance parameter matrix

$$Z = \frac{\begin{pmatrix} z_X(z_Y + z_{XY}) & z_X z_Y \\ z_X z_Y & z_Y(z_X + z_{XY}) \end{pmatrix}}{z_X + z_{XY} + z_Y}$$

- After substitution

$$Z = \begin{pmatrix} 87.27 & 27.27 \\ 27.27 & 77.27 \end{pmatrix}$$

- $A_S = 0.165$

Admittance Parameters

Admittance Parameters

- Admittance parameters are obtained as ratios when one port is short circuited (i.e., $V_1 = 0$ or $V_2 = 0$)
- Feed admittance parameters

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

- ▶ y_{11} is the feed admittance of Port 1 when Port 2 is SC
- ▶ y_{22} is the feed admittance of Port 2 when Port 1 is SC
- ▶ If the network is symmetric $y_{11} = y_{22}$

Admittance Parameters

Admittance Parameters (Contd..)

■ Trans-admittance parameters

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$


- ▶ y_{12} is the TA of the SC current of Port 1 and voltage of Port 2
- ▶ y_{21} is the TI of the SC current of Port 2 and voltage of Port 1
- ▶ If the network is reciprocal $y_{12} = y_{21}$

Admittance Parameters (Contd..)

- The parameter matrix is given by

$$\begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \end{pmatrix}$$

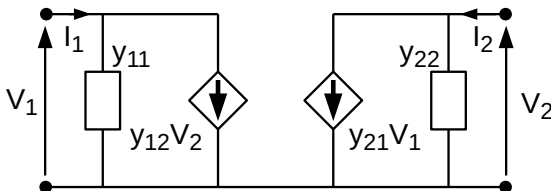- Relates to impedance parameters according to $Y = Z^{-1}$
- Two-port model



Admittance Parameters (Contd..)

- For a terminated network

$$y_{IN} = y_{11} - \left(\frac{y_{12}y_{21}}{y_{22} + y_L} \right)$$

$$y_{OUT} = y_{22} - \left(\frac{y_{12}y_{21}}{y_{11} + y_S} \right)$$

$$A_I = \frac{I_2}{I_1} = \frac{y_{21}y_L}{y_{11}y_L + |Y|}$$

$$A_V = \frac{V_2}{V_1} = \frac{-y_{21}}{y_{22} + y_L}$$

$$A_S = \frac{V_2}{V_S} = \frac{y_{21}y_L}{(y_{11} + y_S)(y_{22} + y_L) - y_{12}y_{21}}$$

Hybrid Parameters

- Hybrid parameters contain a mixture of ratios
 - ▶ Also inverse hybrid parameters aka g parameters ($G = H^{-1}$)
- Both are used for the small signal analysis of amplifiers
 - ▶ The small signal corresponds to a linearization
- Based on the following parameter matrix

$$\begin{pmatrix} V_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{pmatrix} \begin{pmatrix} I_1 \\ V_2 \end{pmatrix}$$

- Input impedance when Port 2 is SC

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

Hybrid Parameters (Contd..)

- Reciprocal of voltage gain when Port 1 is OC

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

- Current gain when Port 2 is SC


$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

- Output admittance when Port 1 is OC

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

Hybrid Parameters (Contd..)

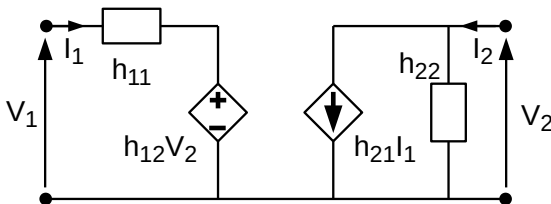- If the network is reciprocal $h_{12} = -h_{21}$
- When the network is symmetrical $h_{11}h_{22} - h_{12}h_{21} = 1$
- Two-port model



Hybrid Parameters (Contd..)

- For a terminated network

$$z_{IN} = h_{11} - \left(\frac{h_{12}h_{21}z_L}{1 + h_{22}z_L} \right)$$

$$z_{OUT} = \frac{z_S + h_{11}}{h_{22}z_S + |H|}$$


$$A_I = \frac{I_2}{I_1} = \frac{h_{21}}{1 + h_{22}z_L}$$

$$A_V = \frac{V_2}{V_1} = \frac{-h_{21}z_L}{h_{11} + |H|z_L}$$

$$A_S = \frac{V_2}{V_S} = \frac{-h_{21}z_L}{(h_{11} + z_S)(1 + h_{22}z_L) - h_{12}h_{21}z_L}$$

ABCD Parameters

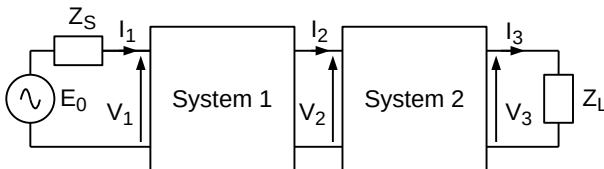- All sets of parameters up to now were suitable for single stage terminated networks
- ABCD parameters are a special set that can be used for the computational analysis of cascading systems
 - ▶ Can model a linear passive component as a 2×2 matrix



ABCD Parameters (Contd..)

- Like hybrid parameters contains a mixture of ratios
- Based on the following parameter matrix with a negative Port 2 current and parameters of a single port per vector

$$\begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix} = \begin{pmatrix} A & B \\ C & D \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix}$$

- This can be alternatively expressed as

$$\begin{pmatrix} V_2 \\ -I_2 \end{pmatrix} = \begin{pmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{pmatrix} \begin{pmatrix} V_1 \\ I_1 \end{pmatrix} = \begin{pmatrix} A' & B' \\ C' & D' \end{pmatrix} \begin{pmatrix} V_1 \\ I_1 \end{pmatrix}$$

where $\mathcal{A} = \mathcal{B}^{-1}$

ABCD Parameters (Contd..)

- Reciprocal of voltage gain when Port 2 is OC

$$a_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

- Trans-impedance when Port 2 is SC

$$a_{12} = \left. -\frac{V_1}{I_2} \right|_{V_2=0}$$

- Trans-admittance when Port 2 is OC

$$a_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

ABCD Parameters (Contd..)

- Reciprocal of current gain when Port 2 is SC

$$a_{22} = -\frac{I_1}{I_2} \bigg|_{V_2=0}$$

- For a reciprocal network $a_{11}a_{22} - a_{12}a_{21} = 1$
- When symmetric $a_{11} = a_{22}$
- When terminated

$$z_{IN} = \frac{a_{11}z_L + a_{12}}{a_{21}z_L + a_{22}}$$

$$z_{OUT} = \frac{a_{12} + a_{22}z_S}{a_{11} + a_{21}z_S}$$

ABCD Parameters (Contd..)

■ Gain ratios


$$A_I = \frac{I_2}{I_1} = \frac{-1}{a_{21}z_L + a_{22}}$$

$$A_V = \frac{V_2}{V_1} = \frac{z_L}{a_{11}z_L + a_{12}}$$

$$A_S = \frac{V_2}{V_S} = \frac{z_L}{(a_{11} + a_{21}z_S)z_L + a_{12} + a_{22}z_S}$$

- **Important Note:** when deriving the expressions for a terminated network for ABCD parameters it is necessary to consider the output current as $(-I_2)$ to prevent a violation of the convention of having a current enter the port of a two-port network.

Cascading

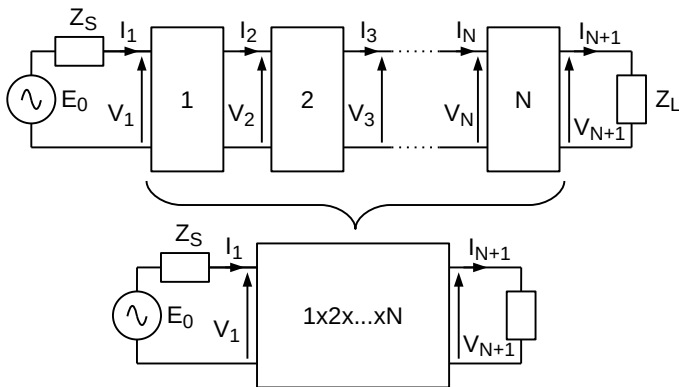

Cascading (Contd..)

- The main importance of ABCD parameters as a circuit analysis and synthesis tool is the ability to cascade multiple systems and simplify as a matrix multiplication

$$\begin{aligned}
 \begin{pmatrix} V_1 \\ I_1 \end{pmatrix} &= \begin{pmatrix} a_{11}^1 & a_{12}^1 \\ a_{21}^1 & a_{22}^1 \end{pmatrix} \begin{pmatrix} V_2 \\ -I_2 \end{pmatrix} \\
 &= \begin{pmatrix} a_{11}^1 & a_{12}^1 \\ a_{21}^1 & a_{22}^1 \end{pmatrix} \begin{pmatrix} a_{11}^2 & a_{12}^2 \\ a_{21}^2 & a_{22}^2 \end{pmatrix} \begin{pmatrix} V_3 \\ -I_3 \end{pmatrix} \\
 &= \mathcal{A}_1 \times \mathcal{A}_2 \times \cdots \times \mathcal{A}_N \begin{pmatrix} V_{N+1} \\ -I_{N+1} \end{pmatrix}
 \end{aligned}$$

Cascading (Contd..)

- Series component \mathcal{A} matrix

$$\mathcal{A}_Z = \begin{pmatrix} 1 & Z \\ 0 & 1 \end{pmatrix} \Rightarrow \mathcal{B}_Z = \begin{pmatrix} 1 & -Z \\ 0 & 1 \end{pmatrix}$$

- Shunt component \mathcal{A} matrix


$$\mathcal{A}_Y = \begin{pmatrix} 1 & 0 \\ Y & 1 \end{pmatrix} \Rightarrow \mathcal{B}_Y = \begin{pmatrix} 1 & 0 \\ -Y & 1 \end{pmatrix}$$

- Using these two matrices an entire circuit can be obtained in its matrix form in the ω or s domain
- The \mathcal{B} form of the matrix allows for the output to be directly obtained without inversion

Cascading (Contd..)

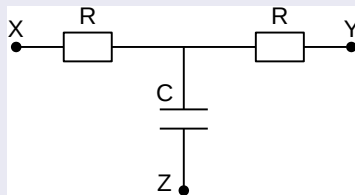Example:

Obtain the \mathcal{A} and \mathcal{B} matrices of the RC T filter given below



Cascading (Contd..)

■ \mathcal{A} matrix

$$\begin{aligned}\mathcal{A} &= \begin{pmatrix} 1 & R \\ 0 & 1 \end{pmatrix} \begin{pmatrix} 1 & 0 \\ j\omega C & 1 \end{pmatrix} \begin{pmatrix} 1 & R \\ 0 & 1 \end{pmatrix} \\ &= \begin{pmatrix} 1 + j\omega RC & 2R + j\omega R^2 C \\ j\omega C & 1 + j\omega RC \end{pmatrix}\end{aligned}$$

■ \mathcal{B} matrix


$$\begin{aligned}\mathcal{B} &= \begin{pmatrix} 1 & -R \\ 0 & 1 \end{pmatrix} \begin{pmatrix} 1 & 0 \\ -j\omega C & 1 \end{pmatrix} \begin{pmatrix} 1 & -R \\ 0 & 1 \end{pmatrix} \\ &= \begin{pmatrix} 1 + j\omega RC & -(2R + j\omega R^2 C) \\ -j\omega C & 1 + j\omega RC \end{pmatrix}\end{aligned}$$

Matrix Estimation


Measurement

- One of the main strengths of the two-port network model is the ability to estimate the matrix from measurements
 - ▶ Measured using ammeters and voltmeters
- Requires the following tests for each port
 - ▶ The open circuit test (output port open circuited)
 - ▶ The short circuit test (output port short circuited)
- The measurement configuration depends upon the input impedance which is initially unknown
 - ▶ Critical only at the extremes
 - ▶ Therefore, can initially take use to estimate the feed impedance and determine the required configuration


The Open Circuit Test

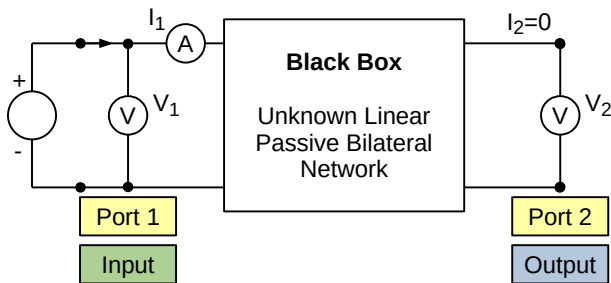

The Short Circuit Test

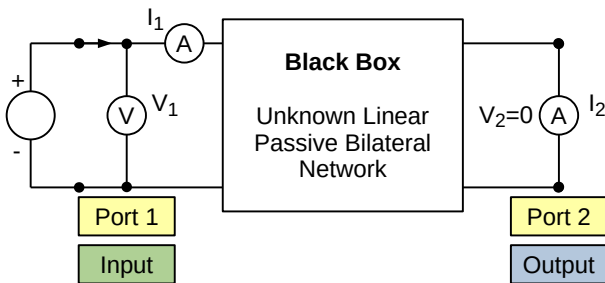


High Impedance Measurement

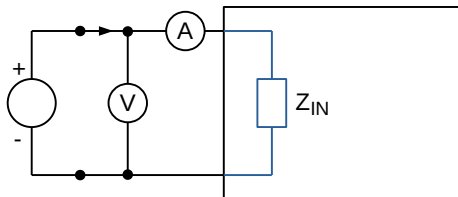

- This configuration is necessary when the feed impedance is comparable to the large impedance of the voltmeter

Low Impedance Measurement

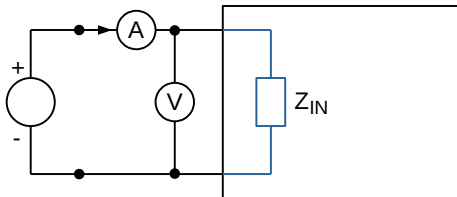

- This configuration is necessary when the feed impedance is comparable to the small impedance of the ammeter

Example 1

Port 1 of an unknown two-port network consisting of a linear passive bilateral network is subjected to an open circuit and short circuit test. The test results are given as follows,

Test	V_1	I_1	V_2	I_2
OC	12 V	40 mA	8 V	0
SC	12 V	72.3 mA	0	(-47.7) mA

Obtain the ABCD parameters of the network.

Example 1 (Contd..)

$$a_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{12}{8} = 1.5$$

$$a_{12} = - \left. \frac{V_1}{I_2} \right|_{V_2=0} = - \frac{12}{(-0.0477)} = 251.6 \, \Omega$$

$$a_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{0.040}{8} = 5 \, \text{mS}$$

$$a_{22} = - \left. \frac{I_1}{I_2} \right|_{V_2=0} = - \frac{0.0723}{(-0.0477)} = 1.5$$

Example 2

The following open circuit test results were obtained for an unknown linear passive bilateral two-port network.

Port	V_1	I_1	V_2	I_2
1	9 V	45 mA	2.25 V	0
2	6 V	0	9 V	120 mA

Determine the impedance parameters of the network.

Example 2 (Contd..)

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{9}{0.045} = 200 \, \Omega$$

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{6}{0.120} = 50 \, \Omega$$

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{2.25}{0.045} = 50 \, \Omega$$

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{9}{0.120} = 75 \, \Omega$$

Conclusion

Conclusion

- Two-port networks provide a measurement based description of a linear bilateral passive circuit
 - ▶ Does not require a thorough analysis
 - ▶ Can be used for analyzing the behavior of the circuit in the frequency or transient (Laplace) domain
 - ▶ Specially the transfer of voltage, current or power
- It can also be used to approximate a black box
- Relates to the formal transfer function of a circuit which maps the input to the output