



**GENERAL SIR JOHN KOTELAWALA DEFENCE UNIVERSITY**

Faculty of Engineering

Department of Electrical, Electronic and Telecommunication Engineering

B.Sc. Engineering Degree

Semester 6 Examination – September 2024

(Intake 39 - EE/ET/MC)

**EE 3213 – POWER ELECTRONICS AND APPLICATIONS I**

Time allowed: 3 Hours

30 September 2024

**INSTRUCTIONS TO CANDIDATES:**

This paper contains 5 questions on 6 pages.

Answer All Questions.

This is a closed book examination.

This examination accounts for 70% of the module assessment. The total maximum mark attainable is 100. The marks assigned for each question & sections thereof are indicated in square brackets.

If you have any doubt as to the interpretation of the wording of a question, make your own decision, but clearly state it on the script.

All Examinations are conducted under the rules & regulations of the University

**DETAILS OF ASSESSMENT:**

This module has 4 LOs, assessed at the end-semester examination

Table below shows LO assessment details

Learning Outcome (LO)	Questions that assess LO	Marks allocated (Total 70%)
LO1	Q1	13
LO2	Q2	17
LO3	Q3, Q4	25
LO4	Q5	15

This Page is Intentionally Left Blank

Question 1

- a) Explain briefly how the Voltage Utilization of a sinusoidal PWM voltage source inverter can be improved by modifying the three sinusoidal reference signals of its modulator.   
 Adding 3<sup>rd</sup> harmonic [03]
- b) Explain briefly why it is necessary to increase the carrier-ratio when delivering low-frequency output voltage by a PWM voltage source inverter operated with constant  $V$  to  $f$  control. [03]
- c) Explain why the sequential control is preferred over the concurrent control for 3-Phase dual-series-bridge thyristor converter for delivering a given combination of output power and voltage. [04]
- d) Explain why the distortion minimization PWM is generally preferred over the harmonic elimination PWM in practice. [03]

Question 2

- a) Three-phase, full-bridge AC to DC diode-converter is operating on 400 V, 50 Hz three-phase AC supply. The converter delivers 15 A constant current to an inductive load. You may ignore the internal impedance of the AC supply. Assume ideal diodes. Determine,
- (i) Mean value of the output DC voltage.  $3\sqrt{2} V_L / \pi$  [02]
- (ii) Peak-peak ripple in the output DC voltage.  $\sqrt{2} V_L - \sqrt{2} V_L \cos 30$  [02]
- (iii) RMS value of the fundamental component of AC side line-current.  $\sqrt{6} I_c / \pi$  [02]
- b) A three-phase voltage source inverter is operated with Voltage Vector PWM at constant sampling frequency 10 kHz. The inverter delivers variable frequency and variable voltage output. Input voltage to the inverter is 750 V DC.
- (i) What is the greatest value of line-voltage fundamental (RMS) obtainable at the output with vector control? [02]
- (ii) The inverter is set to deliver line-line fundamental output voltage of 400 V (rms) of 50Hz. If the 0<sup>th</sup> sampling instant is chosen to coincide with the positive-peak of the desired phase- $a$  voltage, calculate the timing for switching signals  $S_a, S_b$  &  $S_c$  over the sampling-interval after the 75<sup>th</sup> sampling instant. [09]



$$V_a = \frac{1}{2\pi f_s} \int_0^{2\pi} (1 + m \sin 2\pi k - 0.25) d\theta$$

$$V_0 = \frac{3\sqrt{2}}{\pi} \cdot \frac{500 \times 10^{-3} \times 10^4}{10^4}$$



**Question 3**

- a) In order to protect from shoot-through faults, inverters are designed with a blanking-time  $t_B$  for switchover between the upper and the lower IGBTs in each leg. Input DC voltage to the inverter is  $V_d$ . If the inverter is operated with square-wave-PWM at carrier frequency  $f_c$ , show that the step-change in the rms value of fundamental line-line voltage at the output, when over-modulation is used to transfer the control to the square-wave (six-step) control will be given by,

$$m = 1 - 2f_c t_B$$

$$(\Delta V_{line})_{rms} = \frac{2\sqrt{6}V_d f_c t_B}{\pi}$$

[05]

- b) A single-phase VSI with input DC voltage  $V_d$  is delivering an output current  $I_m \sin(\omega t)$  using hysteresis current control within a tolerance band  $\Delta H$ . The load has a resistance  $R$  in series with an inductance  $L$ .

Derive expressions for the switching frequency,

- (i) Near the zero-crossing of the output current.

[05]

- (ii) Near the peak of the output current waveform.

[05]

**Question 4**

A single-phase, full-bridge thyristor converter operating at delay angle  $\alpha$ , delivers constant DC current  $I_o$  to an inductive load. Input sinusoidal AC source has rms voltage  $V_{ph}$ , frequency  $f$ , and internal inductance  $L_s$ .

Show that the mean output voltage  $(V_o)_{mean}$  and the conduction overlap angle  $u$  are given by,

$$(V_o)_{mean} = \left( \frac{2\sqrt{2}V_{ph} \cos \alpha}{\pi} \right) - 4fL_s I_o$$

 $\Delta V_o / \%$ 

[05]

$$u = -\alpha + \cos^{-1} \left( \cos \alpha - \frac{4\pi f L_s I_o}{\sqrt{2}V_{ph}} \right)$$

[05]

$$\frac{A}{\pi}$$


$$(\cos \alpha + \pi/4) - \cos(\alpha - \pi/4)$$

$$\cos \alpha \cos \pi/4 + \sin \alpha \sin \pi/4 - \cos \alpha \cos \pi/4 + \sin \alpha \sin \pi/4$$

$$\frac{1}{\sqrt{2}} \cos \alpha - \frac{\sin \alpha}{\sqrt{2}} - \frac{\cos \alpha}{\sqrt{2}} + \frac{\sin \alpha}{\sqrt{2}}$$

**Question 5**

 - a) Figure Q5 shows a linear DC power supply based on a single-phase bridge-rectifier with capacitor filter.



$$V_i = 230 \text{ V (rms)}$$

$$f = 50 \text{ Hz}$$

$$V_D = 0.7 \text{ V (diode conduction voltage drop)}$$

$$V_S - 2V_D = V_P$$

$$V_o = V_P - \frac{I_o}{4fC}$$

$$\Delta V = \omega C \sqrt{2\Delta V n} \quad 10$$

The power supply needs to deliver output up to 900 mA at nearly 14 V, with peak-peak ripple not exceeding 1.5 V. Design suitable values for,

- (i) Filter capacitance  $C$ . [03]
  - (ii) Transformer turn-ratio  $n_1:n_2$ . [03]
  - (iii) Pulse current rating for each diode. [03]
- b) Construct the power circuits for the following multilevel inverters.
- (i) Three-phase, 5-level, cascaded H-bridge inverter. [02]
  - (ii) Single-phase, 5-level modular multilevel inverter. [02]

Construct the phase-voltage waveform for a 5-level, 3-Phase inverter corresponding to balanced 3-phase square-wave control.

[02]

End of Question Paper