

EE1212- Electronic System I

Lecture 5 - Counters
Capt Geeth Karunaratne

Counters

- Counters can be categorized as synchronous and asynchronous.
- Applications:
 - Control Circuits
 - Signal Generator
 - Timing units


Asynchronous Up Counter

- An asynchronous binary counter is one whose state changes are not controlled by a synchronizing clock pulse (Flip Flops do not operate according to a common clock).
- Counter stage X_i is complemented each time X_{i-1} makes a $1 \rightarrow 0$ transition.
- Stage X_1 is always complemented.

X_n	...	X_3		X_2		X_1
0	...	0		0		0
0	...	0		0		1
0	...	0		1	←	0
0	...	0		1		1
0	...	1	←	0	←	0

Logic Diagram of the Up Counter

Initially all Q outputs are zero.

 

Truth Table & Timing Diagram

Up Counter as frequency divider

- when all the 'J's and 'K's are given '1' as the input, frequency of

$$X_1 = \frac{1}{2} (\text{frequency of clock})$$

$$X_2 = \frac{1}{2} (\text{frequency of } X_1)$$

- Therefore JK flip flops in toggling mode can be viewed as a frequency divider.
- Frequency can be divided by 2^n using n flip flops.

Asynchronous Down Counters

- A down counter is one whose state transitions are reversed from those of the standard counter.

X_n	...	X_3	X_2	X_1
1	...	1	1	1
0	...	0	0	0
0	...	0	0	1
0	...	0	1	0
0	...	0	1	1
0	...	1	0	0


Up count mode

X_n	...	X_3	X_2	X_1
0	...	0	0	0
1	...	1	1	1
1	...	1	1	0
1	...	1	0	1
1	...	1	0	0
1	...	0	1	1

Down count mode

Logic Diagram of the Down Counter

Initially all Q outputs are one.

 

Truth Table & Timing Diagram

Up Down Counter

Example

It is desired to design a binary ripple counter that is capable of counting the number of items passing on a conveyor belt. Each time an item passes a given point, a pulse is generated that can be used as a clock input. If the maximum number of items to be counted is 6000, determine the number of flip-flops required

The counter should be able to count a maximum of 6000 items.

An N-flip-flop would be able to count up to a maximum of $2^N - 1$ counts.

On the 2^N th clock pulse, it will get reset to all 0s.

Now, $2^N - 1$ should be greater than or equal to 6000.

That is, $2^N - 1 \geq 6000$, which gives, $N \geq \log 6001 / \log 2 \geq 3.778 / 0.3010 \geq 12.55$.

The smallest integer that satisfies this condition is 13.

Therefore, the minimum number of flip-flops required=13

Synchronous Counters

- Asynchronous counters are not useful at very high frequencies, especially for counters with large number of bits.
- Another problem caused by propagation delays in asynchronous counts occurs when try to electronically detect (decode) the counter outputs states.
- Both of these problems can be overcome by the use of a synchronous or parallel counter.


Synchronous Counters

- **Synchronous (parallel) counters:** the flip-flops are clocked at the same time by a common clock pulse.
- Clock pulses are applied to the input of all FFs.
- All the flip-flops change state simultaneously (in parallel).

Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J, K inputs).

- $T=0$ or $J=K=0$ (FF does not change state)
- $T=1$ or $J=K=1$ (FF complements)

 Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J, K inputs).



Present state		Next state		Flip-flop inputs	
A_1	A_0	A_1^+	A_0^+	TA_1	TA_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

Example: 2-bit synchronous binary counter (using T flip-flops, or JK flip-flops with identical J, K inputs).

Present state		Next state		Flip-flop inputs	
A_1	A_0	A_1^+	A_0^+	TA_1	TA_0
0	0	0	1	0	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	0	0	1	1

$$TA_1 = A_0$$

$$TA_0 = 1$$

