

Introduction to Verilog HDL

Geeth Karunarathne

Verilog HDL

- Invented by Philip Moorby in 1983/ 1984 at Gateway Design Automation
- Enables specification of a digital system at a range of levels of abstraction: switches, gates, RTL, and higher
- Initially developed in conjunction with the Verilog simulator

Verilog HDL


- Verilog- based synthesis tool introduced by Synopsys in 1987
- Gateway Design Automation bought by Cadence in 1989
- Verilog placed in public domain to compete with VHDL
 - Open Verilog International (OVI) IEEE 1364 -1995 and
 - revised version IEEE 1364 -2001
 - revised version IEEE 1364 -2005

Verilog

- Verilog HDL has a syntax that describes precisely the legal constructs that can be used in the language.
- It uses about 100 keywords pre-defined, lowercase, identifiers that define the language constructs.
- Example of keywords: *module, endmodule, input, output wire, and, or, not* , etc.,
- Any text between two slashes (//) and the end of line is interpreted as a comment.
- Blank spaces are ignored and names are case sensitive.

Module

 
- A *module* is the building block in Verilog.
- It is declared by the keyword *module* and is always terminated by the keyword *endmodule*.
- Each statement is terminated with a semicolon, but there is no semi-colon after *endmodule*.



Module cont..

 Example code

```
module smpl_circuit(A,B,C,x,y);  
  input  A,B,C;  
  output x,y;  
  wire e;  
  and g1(e,A,B);  
  not g2(y,C);  
  or g3(x,e,y);  
endmodule
```




Gate Delays

- Sometimes it is necessary to specify the amount of delay from the input to the output of gates.
- In Verilog, the delay is specified in terms of time units and the symbol **#**.
- The association of a time unit with physical time is made using ***timescale*** compiler directive.
- Compiler directive starts with the “backquote (`)” symbol.
``timescale 1ns/100ps`
- The first number specifies the *unit of measurement* for time delays.
- The second number specifies the *precision* for which the delays are rounded off, in this case to 0.1ns.

```
//Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
    input  A,B,C;
    output x,y;
    wire   e;
    and #(30) g1(e,A,B);
    or  #(20) g3(x,e,y);
    not #(10) g2(y,C);
endmodule
```


Logic Simulation

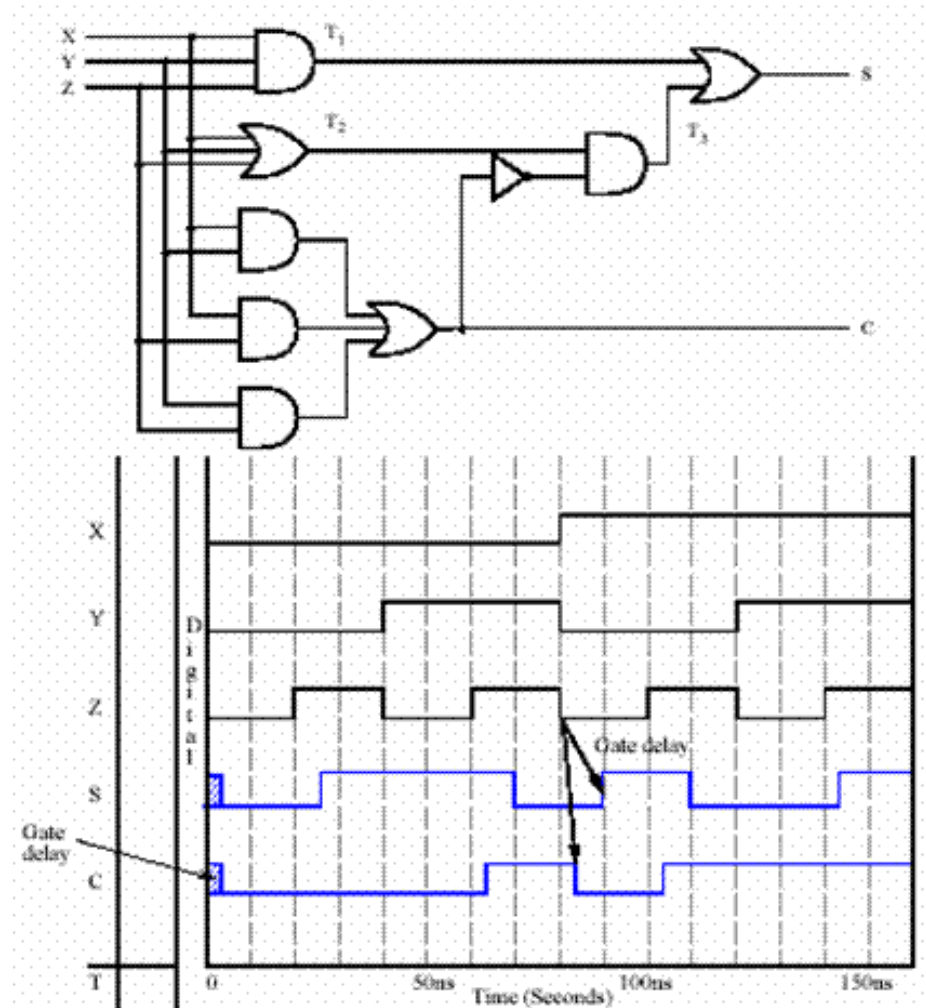- Logic simulation is a fast, accurate method of analyzing a circuit to see its waveforms



Logic Simulation

- In order to simulate a circuit with verilog, it is necessary to apply inputs to the circuit for the simulator to generate an output response.
- A Verilog code that provides the stimulus to a design is called a **test bench**.
- The ***initial*** statement specifies inputs between the keyword ***begin*** and ***end***.
- Initially ABC=000 (A,B and C are each set to 1'b0 (one binary digit with a value 0)).
- **\$finish** is a *system task*.

Verilog Test Bench

```
module circuit_with_delay
(A,B,C,x,y);
  input A,B,C;
  output x,y;
  wire e;
  and #(30) g1(e,A,B);
  or #(20) g3(x,e,y);
  not #(10) g2(y,C);
endmodule
```

```
//Stimulus for simple circuit
module stimcrct;
reg A,B,C;
wire x,y;
circuit_with_delay cwd(A,B,C,x,y);
initial
  begin
    A = 1'b0; B = 1'b0; C = 1'b0;
    #100
    A = 1'b1; B = 1'b1; C = 1'b1;
    #100 $finish;
  end
endmodule
```

Verilog – Simulation

 


Fig. 3-38 Simulation Output of HDL Example 3-3

In the above example, **cwd** is declared as one instance **circuit_with_delay**.

Bitwise Operators

- Bitwise NOT : \sim
- Bitwise AND: $\&$
- Bitwise OR: $|$
- Bitwise XOR: \wedge
- Bitwise XNOR: $\sim\wedge$ or $\wedge\sim$

Boolean Expressions:

- These are specified in Verilog with a continuous assignment statement consisting of the keyword *assign* followed by a Boolean Expression.
- The earlier circuit can be specified using the statement:

```
assign x = (A&B) | ~C)
```

E.g. $x = A + BC + B'D$

$$y = B'C + BC'D'$$

E.g. $x = A + BC + B'D$

$y = B'C + BC'D'$

//Circuit specified with Boolean equations

```
module circuit_bln (x,y,A,B,C,D);
```

```
    input A,B,C,D;
```

```
    output x,y;
```

```
    assign x = A | (B & C) | (~B & C);
```

```
    assign y = (~B & C) | (B & ~C & ~D);
```

```
endmodule
```


Types of Modelling in Verilog

- A Verilog code can be written in the following styles:
 1. Structural style
 - i. Gate Level Modeling
 - ii. Module Instantiation
 2. Dataflow style
 3. Behavioral style
 4. Mixed style

Gate-Level Modeling

- Circuit is specified by its **logic gates** and their **interconnections**.
- It provides a textual description of a schematic diagram.
- Verilog recognizes 12 basic gates as predefined primitives.
 - 4 primitive gates of 3-state type (bufif0, bufif1, notif0 and notif1).
 - Other 8 are: **and, nand, or, nor, xor, xnor, not, buf**
- When the gates are simulated, the system assigns a four-valued logic set to each gate – *0, 1, unknown (x) and high impedance (z)*

Gate-level modeling

- When a primitive gate is incorporated into a module, we say it is *instantiated* in the module.
- statements that reference lower-level components in the design, essentially creating unique copies (or *instances*) of those components in the higher-level module.
- A module that uses a gate in its description is said to *instantiate* the gate.

Modeling with vector data (multiple bit widths)

- A vector is specified within square brackets and two numbers separated with a colon.

e.g. **output** [0 : 3] D; - This declares an output vector D with 4 bits, 0 through 3.

wire [7 : 0] SUM; – This declares a wire vector SUM with 8 bits numbered 7 through 0.

The first number listed is the most significant bit of the vector.


Gate-level Modeling

- Two or more modules can be combined to build a hierarchical description of a design.
- There are two basic types of design methodologies.
 - **Top down:** In top-down design, the top level block is defined and then sub-blocks necessary to build the top level block are identified.
 - **Bottom up:** Here the building blocks are first identified and then combine to build the top level block.
- In a top-down design, a 4-bit binary adder is defined as top-level block with 4 full adder blocks. Then we describe two half-adders that are required to create the full adder.
- In a bottom-up design, the half-adder is defined, then the full adder is constructed and the 4-bit adder is built from the full adders.


Gate-level Modeling

- A bottom-up hierarchical description of a 4-bit adder is described in Verilog as
 - Half adder: defined by instantiating primitive gates.
 - Then define the full adder by instantiating two half-adders.
 - Finally the third module describes 4-bit adder by instantiating 4 full adders.
- **Note:** In Verilog, one module definition cannot be placed within another module description.

Half Adder

 
 
$$(a) \begin{aligned} S &= xy' + x'y \\ C &= xy \end{aligned}$$



$$(b) \begin{aligned} S &= x \oplus y \\ C &= xy \end{aligned}$$

4-bit Full Adder

 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

 


Fig. 4-9 4-Bit Adder

4-bit Full Adder

//Gate-level hierarchical description of 4-bit adder

```
module halfadder (S,C,x,y);
```

```
    input x,y;
```

```
    output S,C;
```

```
    //Instantiate primitive gates
```

```
    xor (S,x,y);
```

```
    and (C,x,y);
```

```
endmodule
```

```
module fulladder (S,C,x,y,z);
```

```
    input x,y,z;
```

```
    output S,C;
```

```
    wire S1,D1,D2; //Outputs of first XOR and two AND  
gates
```

```
    //Instantiate the half adders
```

```
    halfadder HA1(S1,D1,x,y), HA2(S,D2,S1,z);
```


```
    or g1(C,D2,D1);
```

```
endmodule
```

4-bit Full Adder

```
module 4bit_adder (S,C4,A,B,C0);  
    input [3:0] A,B;  
    input C0;  
    output [3:0] S;  
    output C4;  
    wire C1,C2,C3;    //Intermediate carries  
  
    //Instantiate the full adder  
    fulladder FA0 (S[0],C1,A[0],B[0],C0),  
                FA1 (S[1],C2,A[1],B[1],C1),  
                FA2 (S[2],C3,A[2],B[2],C2),  
                FA3 (S[3],C4,A[3],B[3],C3);  
  
endmodule
```

2 to 4 Decoder

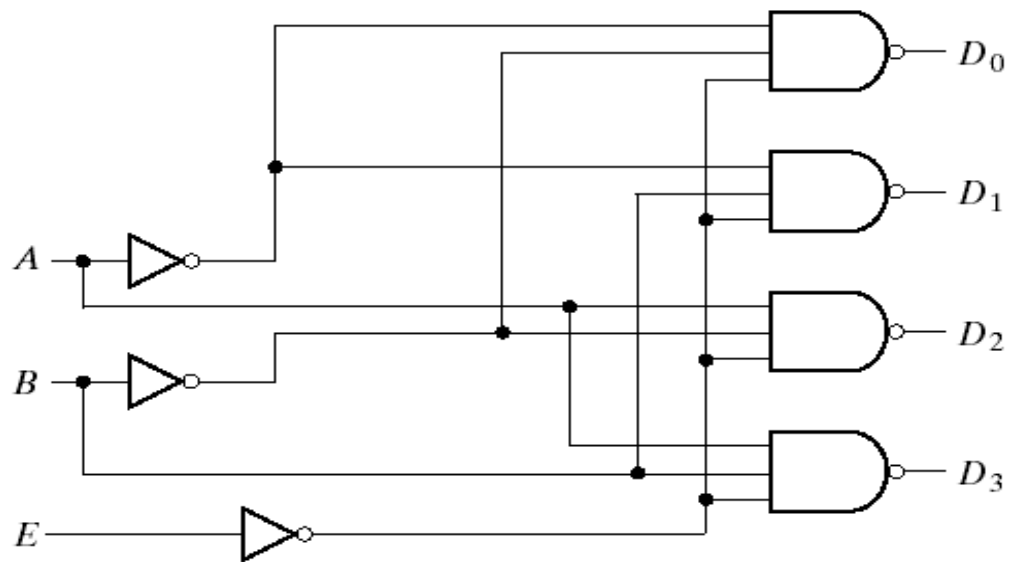

(a) Logic diagram


E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table


2 to 4 Decoder

```
//Gate-level description of a 2-to-4-line decoder
module decoder_gl (A,B,E,D);
    input    A,B,E;
    output [0:3] D;
    wire     Anot,Bnot,Enot;
    not
        n1 (Anot,A) ,
        n2 (Bnot,B) ,
        n3 (Enot,E) ;
    nand
        n4 (D[0],Anot,Bnot,Enot) ,
        n5 (D[1],Anot,B,Enot) ,
        n6 (D[2],A,Bnot,Enot) ,
        n7 (D[3],A,B,Enot) ;
endmodule
```


Three-State Gates

 


bufifl

 

bufif0

 

notifl

 


notif0

Three-State Gates

- Three-state gates have a control input that can place the gate into a high-impedance state. (symbolized by **z** in verilog).
- The **bufif1** gate behaves like a normal buffer if `control=1`. The output goes to a high-impedance state **z** when `control=0`.
- **bufif0** gate behaves in a similar way except that the high-impedance state occurs when `control=1`
- Two **not** gates operate in a similar manner except that the o/p is the complement of the input when the gate is not in a high impedance state.
- The gates are instantiated with the statement
 - `gate name (output, input, control);`

Three-State Gates

 The output of 3-state gates can be connected together to form a common output line. To identify such connections, verilog uses the keyword tri (for tri-state) to indicate that the output has multiple drivers.



```
module muxtri (A,B,sel,out);  
  input      A,B,sel;  
  output     OUT;  
  tri        OUT;  
  bufif1     (OUT,A,sel);  
  bufif0     (OUT,B,sel);  
endmodule
```

Dataflow Modeling

- Dataflow modeling uses a number of operators that act on operands to produce desired results.
- Verilog provides about 30 operator types.
- Dataflow modeling uses continuous assignments and the keyword **assign**.
- A continuous assignment is a statement that assigns a value to a net.
- The value assigned to the net is specified by an expression that uses operands and operators.

Dataflow Modeling

//Dataflow description of a 2-to-4-line decoder

```
module decoder_df (A,B,E,D);  
    input A,B,E;  
    output [0:3] D;  
    assign D[0] = ~(~A & ~B & ~E),  
           D[1] = ~(~A & B & ~E),  
           D[2] = ~(A & ~B & ~E),  
           D[3] = ~(A & B & ~E);  
endmodule
```

A 2-to-1 line multiplexer with data inputs A and B, select input S, and output Y is described with the continuous assignment

```
assign Y = (A & S) | (B & ~S)
```

Dataflow Modeling

```
//Dataflow description of 4-bit adder
module binary_adder (A,B,Cin,SUM,Cout);
    input [3:0] A,B;
    input Cin;
    output [3:0] SUM;
    output Cout;
    assign {Cout,SUM} = A + B + Cin;
endmodule
```

```
//Dataflow description of a 4-bit comparator.
module magcomp (A,B,ALTB,AGTB,AEQB);
    input [3:0] A,B;
    output ALTB,AGTB,AEQB;
    assign ALTB = (A < B),
           AGTB = (A > B),
           AEQB = (A == B);
endmodule
```

Dataflow Modeling

- The addition logic of 4 bit adder is described by a single statement using the operators of addition and concatenation.
- The plus symbol (+) specifies the binary addition of the 4 bits of **A** with the 4 bits of **B** and the one bit of **Cin**.
- The target output is the concatenation of the output carry **Cout** and the four bits of **SUM**.
- Concatenation of operands is expressed within braces and a comma separating the operands. Thus, {**Cout**, **SUM**} represents the 5-bit result of the addition operation.

Dataflow Modeling

- Dataflow Modeling provides the means of describing combinational circuits by their function rather than by their gate structure.
- **Conditional operator (?:)**
condition ? true-expression : false-expression;
- A 2-to-1 line multiplexer
assign OUT = select ? A : B;

```
//Dataflow description of 2-to-1-line mux
module mux2x1_df (A,B,select,OUT);
    input A,B,select;
    output OUT;
    assign OUT = select ? A : B;
endmodule
```

Behavioral Modeling


- Behavioral modeling represents digital circuits at a functional and algorithmic level.
- It is used mostly to describe sequential circuits but can also be used to describe combinational circuits.
- Behavioral descriptions use the keyword **always** followed by a list of procedural assignment statements.
- The target output of procedural assignment statements must be of the **reg** data type.
- A **reg** data type retains its value until a new value is assigned.

Behavioral Modeling

- The procedural assignment statements inside the **always** block are executed every time there is a change in any of the variable listed after the @ symbol. (Note that there is no “;” at the end of **always** statement)

```
//Behavioral description of 2-to-1-line multiplexer
module mux2x1_bh(A,B,select,OUT);
    input A,B,select;
    output OUT;
    reg OUT;
    always @(select or A or B)
        if (select == 1) OUT = A;
        else OUT = B;
endmodule
```

Behavioral Modeling

 

(a) Logic diagram

s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

4-to-1 line
multiplexer

Behavioral Modeling

//Behavioral description of 4-to-1 line mux

```
module mux4x1_bh (i0,i1,i2,i3,select,y);  
    input i0,i1,i2,i3;  
    input [1:0] select;  
    output y;  
    reg y;  
    always @(i0 or i1 or i2 or i3 or select)  
        case (select)  
            2'b00: y = i0;  
            2'b01: y = i1;  
            2'b10: y = i2;  
            2'b11: y = i3;  
        endcase  
endmodule
```


Behavioral Modeling

- In 4-to-1 line multiplexer, the select input is defined as a 2-bit vector and output y is declared as a reg data.
- The always block has a sequential block enclosed between the keywords **case** and **endcase**.
- The block is executed whenever any of the inputs listed after the @ symbol changes in value.

Structural code

Ex1:

```
module mynand (x, a, b);  
  input a, b;  
  output x;  
  wire y;  
  
  and A1 (y,a,b);  
  not A2 (x,y);  
  
endmodule
```

Data Flow code

Ex2:

```
module mynand (x, a, b);  
  input a, b;  
  output x;  
  
  assign y = (a==1 & b==1)?1:0;  
  assign x = (y==0)?1:0;  
  
endmodule
```

Writing a Test Bench

- A test bench is an verilog program used for applying stimulus to an verilog design in order to test it and observe its response during simulation.
- In addition to the always statement, test benches use the **initial** statement to provide a stimulus to the circuit under test.
- The **always** statement executes repeatedly in a loop. The initial statement executes only once starting from simulation time=0 and may continue with any operations that are delayed by a given number of units as specified by the symbol #.

Writing a Test Bench

```
initial begin  
    A=0; B=0;  
    #10 A=1;  
    #20 A=0; B=1;  
end
```

- The block is enclosed between **begin** and **end**. At time=0, A and B are set to 0. 10 time units later, A is changed to 1. 20 time units later (at t=30) a is changed to 0 and B to 1.

Writing a Test Bench

- Inputs to a 3-bit truth table can be generated with the initial block

```
initial begin  
    D = 3'b000;  
    repeat (7);  
        #10 D = D + 3'b001;  
end
```

- The 3-bit vector D is initialized to 000 at time=0. The keyword **repeat** specifies looping statement: one is added to D seven times, once every 10 time units.

Writing a Test-Bench

- A stimulus module is an verilog program that has the following form.

module testname

*Declare local **reg** and **wire** identifiers*

Instantiate the design module under test.

*Generate stimulus using **initial** and **always** statements*

Display the output response.

endmodule

- A test module typically has no inputs or outputs.
- The signals that are applied as inputs to the design module for simulation are declared in the stimulus module as local reg data type.
- The outputs of the design module that are displayed for testing are declared in the stimulus model as local wire data type.
- The module under test is then instantiated using the local identifiers.

Writing a Test-Bench

- The response to the stimulus generated by the **initial** and **always** blocks will appear at the output of the simulator as timing diagrams.
- It is also possible to display numerical outputs using Verilog *system tasks*.
 - **\$display** – display one-time value of variables or strings with end-of-line return,
 - **\$write** – same \$display but without going to next line.
 - **\$monitor** – display variables whenever a value changes during simulation run.
 - **\$time** – displays simulation time
 - **\$finish** – terminates the simulation
- The syntax for **\$display**, **\$write** and **\$monitor** is of the form
Task-name (format-specification, argument list);
E.g. **\$display**(%d %b %b, C,A,B);
\$display("time = %0d A = %b B=%b",**\$time**,A,B);

Writing a Test-Bench

```
//Dataflow description of 2-to-1-line multiplexer
```

```
module mux2x1_df (A,B,select,OUT);
```

```
    input A,B,select;
```

```
    output OUT;
```

```
    assign OUT = select ? A : B;
```

```
endmodule
```


Writing a Test-Bench

```
//Stimulus for mux2x1_df
module testmux;
    reg TA,TB,TS;    //inputs for mux
    wire Y;          //output from mux
    mux2x1_df mx (TA,TB,TS,Y);    // instantiate mux
    initial begin
        $monitor("select=%b A=%b B=%b OUT=%b",TS,TA,TB,Y);
        TS = 1; TA = 0; TB = 1;
        #10 TA = 1; TB = 0;
        #10 TS = 0;
        #10 TA = 0; TB = 1;
    end
endmodule
```

4-to-1 Multiplexer

 


Fig. 3-19 4-to-1-Line Multiplexer

4-to-1 Multiplexer

```
//4-to-1 Mux: Structural Verilog
module mux_4_to_1_st_v(S,D,Y);
    input  [1:0]S;
    input  [3:0]D;
    output Y;
    wire  [1:0]not_s;
    wire  [0:3]N;
    not g0(not_s[0],S[0]),g1(not_s[1],S[1]);
    and g2(N[0],not_s[0],not_s[1],D[0]),
        g3(N[1],S[0],not_s[1],D[0]),
        g4(N[2],not_s[0],S[1],D[0]),
        g5(N[3],S[0],S[1],D[0]);
    or g5(Y,N[0],N[1],N[2],N[3]);
endmodule
```

4-to-1 Multiplexer – Data Flow

```
//4-to-1 Mux: Dataflow description
module mux_4_to_1(S,D,Y);
    input [1:0]S;
    input [3:0]D;
    output Y;
    assign Y = (~S[1]&~S[0]&D[0]) | (~S[1]&S[0]&D[1])
               | (S[1]&~S[0]&D[2]) | (S[1]&S[0]&D[3]);
endmodule
```

```
//4-to-1 Mux: Conditional Dataflow description
module mux_4_to_1(S,D,Y);
    input [1:0]S;
    input [3:0]D;
    output Y;
    assign Y = (S==2'b00)?D[0] : (S==2'b01)?D[1] :
               (S==2'b10)?D[2] : (S==2'b11)?D[3]:1'bx;;
endmodule
```

4-to-1 Multiplexer

```
//4-to-1 Mux: Dataflow Verilog Description
module mux_4_to_1(S,D,Y);
    input  [1:0]S;
    input  [3:0]D;
    output Y;
    assign Y=S[1]?(S[0]?D[3]:D[2]):(S[0]?D[1]:D[0]);
endmodule
```