



General Sir John Kotelawala Defense University
Basic Electronics
Tutorial 3 – Transistors

Question 1

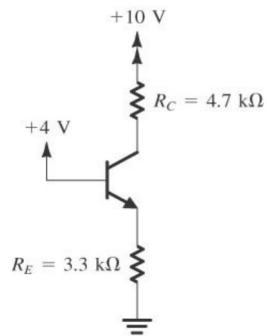


Figure 1

Determine I_B , I_C , and V_C for $\alpha = 0.99$. Assume the transistor to be of silicon.

Question 2

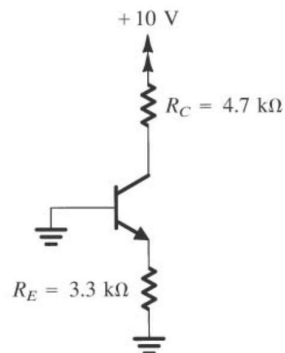


Figure 2

Determine I_B , I_C , V_E and V_C .

Question 3

Determine $I_{C(\text{sat})}$ for the transistor in Figure 3. What is the value of I_B necessary to produce saturation? What minimum value of V_{IN} is necessary for saturation? ($\beta = 150$)



General Sir John Kotelawala Defense University
Basic Electronics
Tutorial 3 – Transistors

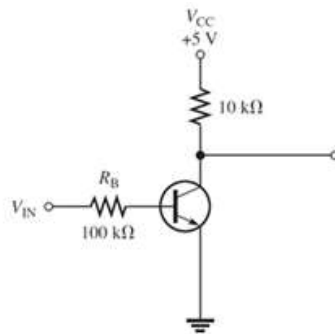


Figure 3

Question 4

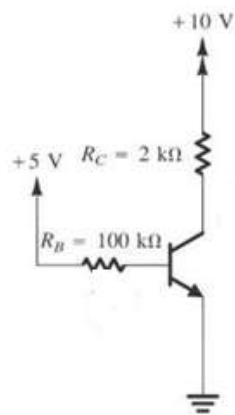


Figure 4

Determine I_B , I_C , I_E and V_C for $\alpha = 100$. Assume the transistor to be of silicon.

Question 5

Complete the design of the fixed-biased transistor circuit shown by determining R_C and R_B for a Q-point of $I_C = 6\text{mA}$ and $V_{CE} = 4\text{V}$. The transistor forward current gain is $\beta = 200$ with a $V_{BE} = 0.7\text{V}$.



General Sir John Kotelawala Defense University
Basic Electronics
Tutorial 3 – Transistors

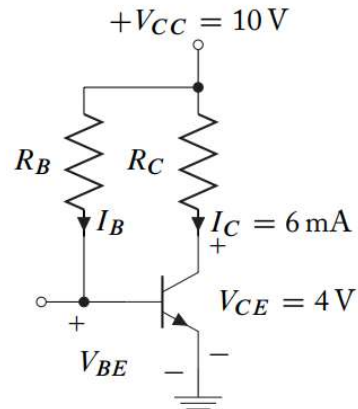


Figure 5

Question 6

Find the operating point (V_{CE} , I_B and I_C) for the emitter biased circuit with two power supplies shown in Figure 6. Let $V_{BE} = 0.84\text{V}$, $\beta = 200$.

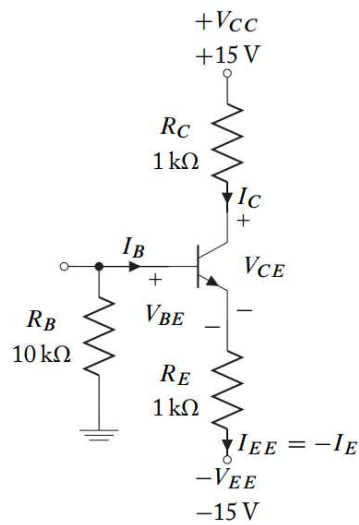


Figure 6