



GENERAL SIR JOHN KOTELAWALA DEFENCE UNIVERSITY
Faculty of Engineering
Department of Electrical, Electronic and Telecommunication Engineering

B.Sc. Engineering Degree
Semester 6 Examination – January 2021
(Intake 35 - EE/ET/MC)

EE 3223 – POWER ELECTRONICS AND APPLICATIONS I

Time allowed: 3 Hours

02 February 2021

INSTRUCTIONS TO CANDIDATES:

This paper contains 6 questions on 5 pages.
Answer any FIVE Questions only.
This is a closed book examination.

This examination accounts for 80% of the module assessment. The total maximum mark attainable is 100. The marks assigned for each question & sections thereof are indicated in square brackets.

If you have any doubt as to the interpretation of the wording of a question, make your own decision, but clearly state it on the script.

All Examinations are conducted under the rules & regulations of the University

Question 1

- a) (i) Describe briefly the strengths and weaknesses of the thyristor as a power switching device. [03]
 (ii) Why is the IGBT popular in most of the present day power switching applications? [03]
 (iii) How do you compare IGBT with Power MOSFET? [03]
- b) An IGBT in a certain converter is required to switch inductive load current of 20A at 10 kHz with a maximum switching duty factor of 0.9. Converter voltage is 500V DC. The following data are available for the IGBT in this application:
- | | |
|---|----------------------|
| Conduction voltage drop | = 1.8 V |
| Turn on transient time | = 0.2 μ s |
| Turn off transient time | = 0.8 μ s |
| Junction-to-Case thermal resistance | = 0.4 $^{\circ}$ C/W |
| Case-to-sink contact thermal resistance | = 0.1 $^{\circ}$ C/W |
| Ambient temperature | = 35 $^{\circ}$ C |
| Specified maximum junction temperature | = 135 $^{\circ}$ C |
- (i) Determine the thermal resistance of the required heat sink. [08]
 (ii) What is the Case temperature of the IGBT for the heat sink in (i) above? [03]

Question 2

- a) Figure Q2 shows a linear DC power supply based on a single-phase bridge-rectifier with capacitor filter.


 


Figure Q2

 $R = 15 \Omega$
 $C = 6000 \mu\text{F}$
 $n_1:n_2 = 18:1$
 $V_1 = 230 \text{ V (rms)}$
 $f = 50 \text{ Hz}$
 $V_D = 0.7 \text{ V (diode conduction voltage drop)}$



Estimate,

- (i) Mean value of output voltage V_o . 15.79 [04]
 (ii) Peak-peak ripple in output voltage. 45.572 3.158V [02]
 (iii) Peak value of diode current. 19.014 [04]
- b) A three phase full-bridge diode-converter is operating on 400 V, 50 Hz, three phase AC supply. It delivers 6 kW of power to an inductive load. Assume that the output current is continuous and having negligible ripple. Determine,
- (i) Mean value of output DC voltage. 661.5V [04]
 (ii) Peak-peak ripple in output voltage 75.38 [02]
 (iii) RMS value of the fundamental component of line current at the input. [04]

Question 3

- a) A three phase full-bridge thyristor converter is operating on 400 V, 50 Hz, three phase AC supply. It delivers 9 kW of power to an inductive load at 380 V DC (mean). Supply side inductance is 3 mH per phase. You may assume that the output current is continuous and ripple free.

Calculate,

- (i) Delay (firing) angle. 46.68° [04]
 (ii) Conduction overlap angle. 7.66° [04]
 (iii) RMS value of the fundamental component of input line current. $18.426 A$ [04]

- b) For the converter in (a) above, sketch the following waveforms indicating appropriate values.

- (i) Output voltage. [04]
 (ii) One of the line-line voltage waveforms at the converter input (PCC). [04]

Question 4

- a) Unipolar, sinusoidal PWM control with carrier-ratio 54, depth of modulation 0.8 and reference frequency 50 Hz is applied on a single-phase VSI, which is fed at 300 V DC input.

- (i) Sketch the arrangement of the PWM modulator. [03]
 (ii) Determine the RMS value of the fundamental component of output voltage. [03]
 (iii) What is the lowest order significant harmonic present in the output voltage? [03]
 (iv) What is the switching frequency? $2700 Hz$ [02]

- b) Regular sampled PWM control is applied on a three-phase VSI with a depth of modulation 0.65, carrier ratio 75, and reference frequency 50 Hz. Calculate the timing instant. Take the 0th sampling point to coincide with a positive-going zero-crossing of phase-A reference signal. [09]

Question 5

- a) A single-phase VSI with input DC voltage V_d is delivering an output current $I_m \sin(\omega t)$ using hysteresis current control within a tolerance band ΔH . The load comprises a resistance R and inductance L in series. Derive expressions for the maximum and the minimum switching frequencies during one cycle of output current. Assume the peak, respectively, of the reference current. [10]

- b) Voltage vector PWM is applied on a three-phase VSI at a sampling frequency 5 kHz, to deliver 50 Hz fundamental output voltage. Input voltage to the inverter is 750 V DC. Determine the timing for switching signals S_a , S_b & S_c over the sampling interval when the sampled values of desired voltages V_a , V_b & V_c for three phases are -400 V 250 V and 150 V respectively.

Question 6

- a) Three-phase VSI shown in Figure Q6(a) is controlled using sinusoidal PWM to deliver a specified combination of real-power (P) and reactive-power (Q) to the grid. Three-phase reference signals for the PWM modulator are derived through vector control and Figure Q6(b) shows inverter voltage vector \bar{V}_I , inverter current vector \bar{I} and the grid-voltage vector \bar{V}_G . Synchronously rotating d -axis is chosen to coincide with the direction of \bar{V}_G and the d & q components of different vectors are as shown in the Figure.

- (i) State magnitude V_{gd} of the grid-voltage vector in terms of the grid line-voltage RMS value V_L . [02]
- (ii) Give the set values $(I_d)_{SET}$ and $(I_q)_{SET}$ in terms of P , Q and V_L . [04]
- (iii) Show that,

$$V_{Id} = L \frac{dI_d}{dt} - \omega L I_q + V_{gd}$$

$$V_{Iq} = L \frac{dI_q}{dt} + \omega L I_d$$

Where, ω is angular frequency of grid voltage and L is inductance per phase of the interconnection. [07]

- b) Draw a block diagram to show how the three-phase reference signals for the sinusoidal PWM modulator are generated using the inputs of $(I_d)_{SET}$, $(I_q)_{SET}$ and feedback grid voltages v_{ga} , v_{gb} and v_{gc} . [07]

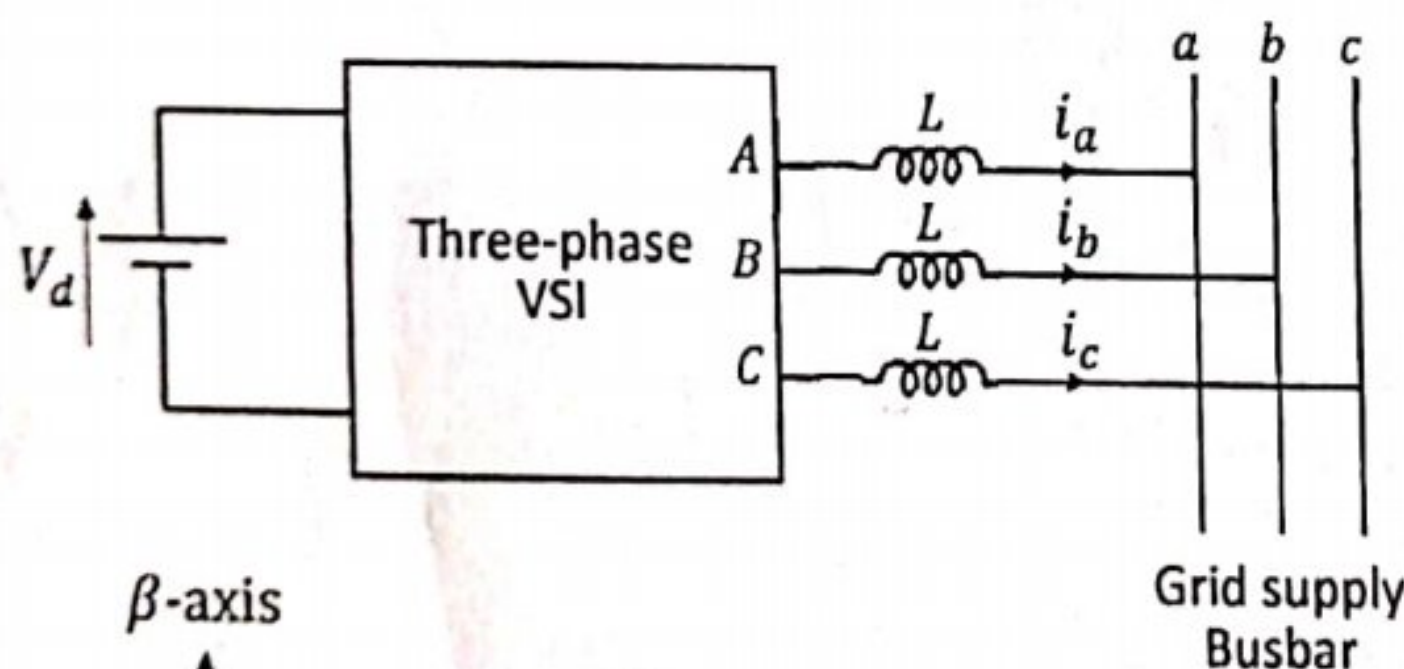


Fig. Q6(a)

 


Fig. Q6(b)

End of Question Paper