

Lecture 1 - Introduction



ET3233 - Digital Systems Design

Geeth Karunaratne



Module Outline

1. Hardware Description Languages
2. RTL Based System Design
3. RISC Architecture
4. Processor Design
5. Memory Design
6. Design of an ALU
7. Asynchronous Sequential System Design

Digital Logic

1 and **0**

Boolean Algebra - Axioms

(A1) $X = 0$ If $X \neq 1$

(A1') $X = 1$ If $X \neq 0$

(A2) If $X = 0$, then $X' = 1$

(A2') If $X = 1$, then $X' = 0$

(A3) $0 \cdot 0 = 0$

(A3') $1 + 1 = 1$

(A4) $1 \cdot 1 = 1$

(A4') $0 + 0 = 0$

(A5) $0 \cdot 1 = 1 \cdot 0 = 0$

(A5') $1 + 0 = 0 + 1 = 1$

Single Variable Theorems

(T1)	$X + 0 = X$	(T1')	$X \cdot 1 = X$	(Identities)
(T2)	$X + 1 = 1$	(T2')	$X \cdot 0 = 0$	(Null elements)
(T3)	$X + X = X$	(T3')	$X \cdot X = X$	(Idempotency)
(T4)	$(X')' = X$			(Involution)
(T5)	$X + X' = 1$	(T5')	$X \cdot X' = 0$	(Complements)

*All the above theorems involves Boolean rules related to a single variable "X", hence called single variable theorems.

Multiple Variable Theorems


(T6)	$X + Y = Y + X$	(T6')	$X \cdot Y = Y \cdot X$	(Commutativity)
(T7)	$(X + Y) + Z = X + (Y + Z)$	(T7')	$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$	(Associativity)
(T8)	$X \cdot Y + X \cdot Z = X \cdot (Y + Z)$	(T8')	$(X + Y) \cdot (X + Z) = X + Y \cdot Z$	(Distributivity)
(T9)	$X + X \cdot Y = X$	(T9')	$X \cdot (X + Y) = X$	(Covering)
(T10)	$X \cdot Y + X \cdot Y' = X$	(T10')	$(X + Y) \cdot (X + Y') = X$	(Combining)
(T11)	$X \cdot Y + X' \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$	(T11')	$(X + Y) \cdot (X' + Z) \cdot (Y + Z) = (X + Y) \cdot (X' + Z)$	(Consensus)

* Above theorems involve Boolean rules related to two or three variables, hence called multiple variable theorems.


Transistor Fabrication

D Transistor fabrication in silicon chips

Traditional Planar Transistor

 

22 nm Tri-Gate Transistor

 


How are microchips made?

From sand to semiconductors

Transistor as a Switch

 - D NOR gate implementation using transistors.



Logic Circuit Design

Combinational Logic

Output is only a function of the current inputs.

They are stateless.

Sequential Logic

The output of Sequential logic circuits depends on BOTH current inputs and previous inputs.


Sequential Logic circuits have memory due to this property.

Logic Circuit Design


Combinational Logic

Output is only a function of the current inputs.

They are stateless.

 


$$\text{Output} = F(\text{Inputs})$$

 

$$Y = F(A, B, C)$$

Logic Circuit Design

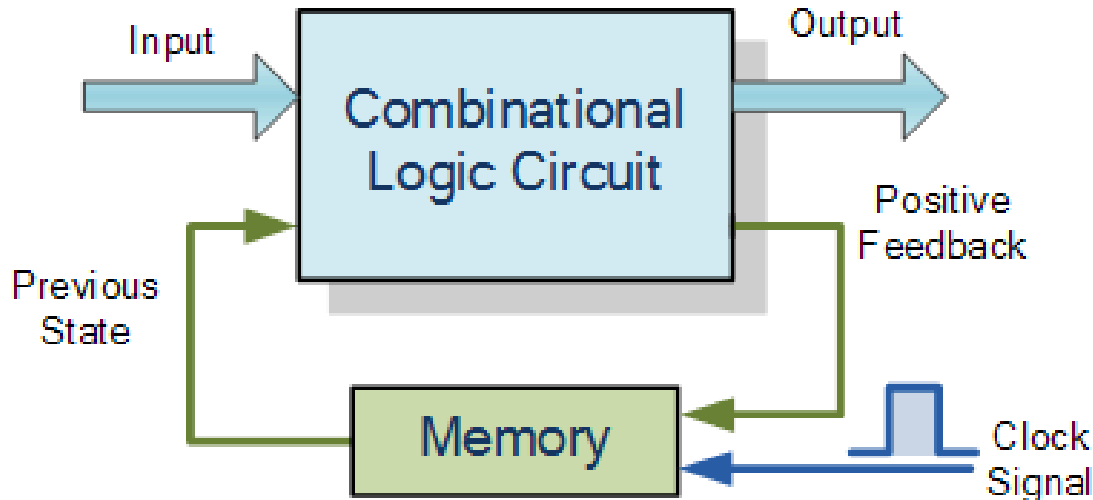

Sequential Logic

The output of Sequential logic circuits depends on BOTH current inputs and previous inputs.



Sequential Logic circuits have memory due to this property.

Combinational Logic Examples


- D Enabling Circuits
- D Encoder
- D Decoder
- D Multiplexer
- D Demultiplexer
- D Comparator
- D Adder/ Subtractor

Multiplexer (MUX)

  - D Combinational circuit that selects binary data from one of many input lines to the output line.
- D Multiplexer is also known as Data Selector.




2 to 1 Multiplexer

 

Truth Table

S	F
0	A
1	B



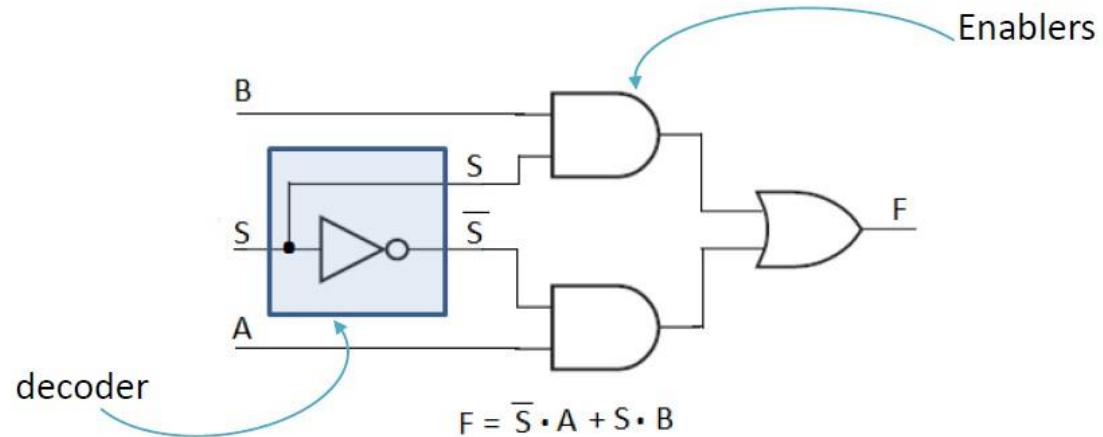
*Abbreviated Truth Table
Inputs A,B listed in output column*



Full Adder

Truth Table


C_{IN}	X	Y	C_{OUT}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

   

Full adder: (a) gate level circuit diagram; (b) logic symbol; (c) alternate logic symbol suitable for cascading.

Ripple Carry Adder

 
- Several full adders could be cascaded to make a ripple carry adder.
 - Four Bit Ripple Carry Adder



Sequential Logic Examples

- D Latches
- D Flip Flops
- D Counters
- D Registers


Latches - D Latch

 


(a) circuit design using NAND gates

C	D	Q	QN
1	0	0	1
1	1	1	0
0	x	last Q	last QN

(b) function table

 


(c) logic symbol

 

Functional behavior of a D latch for various inputs.

Flip Flops - D Flip Flop


Positive-edge-triggered D flip-flop:

 


(a) circuit design using D latches

D	CLK	Q	QN
0		0	1
1		1	0
x	0	last Q	last QN
x	1	last Q	last QN

(b) function table


 


(c) logic symbol

 


Divide by 2 Counter

  - D The divide by two counter is the simplest counter which can only count up to 1 before it resets.
- D This counter could also be used as a frequency divider which divide the input frequency by 2.




3-bit Ripple Counter

 - D A **n**-bit ripple counter could count up to a maximum of $2^n - 1$.
- D The 3-bit ripple counter can count up to 7.



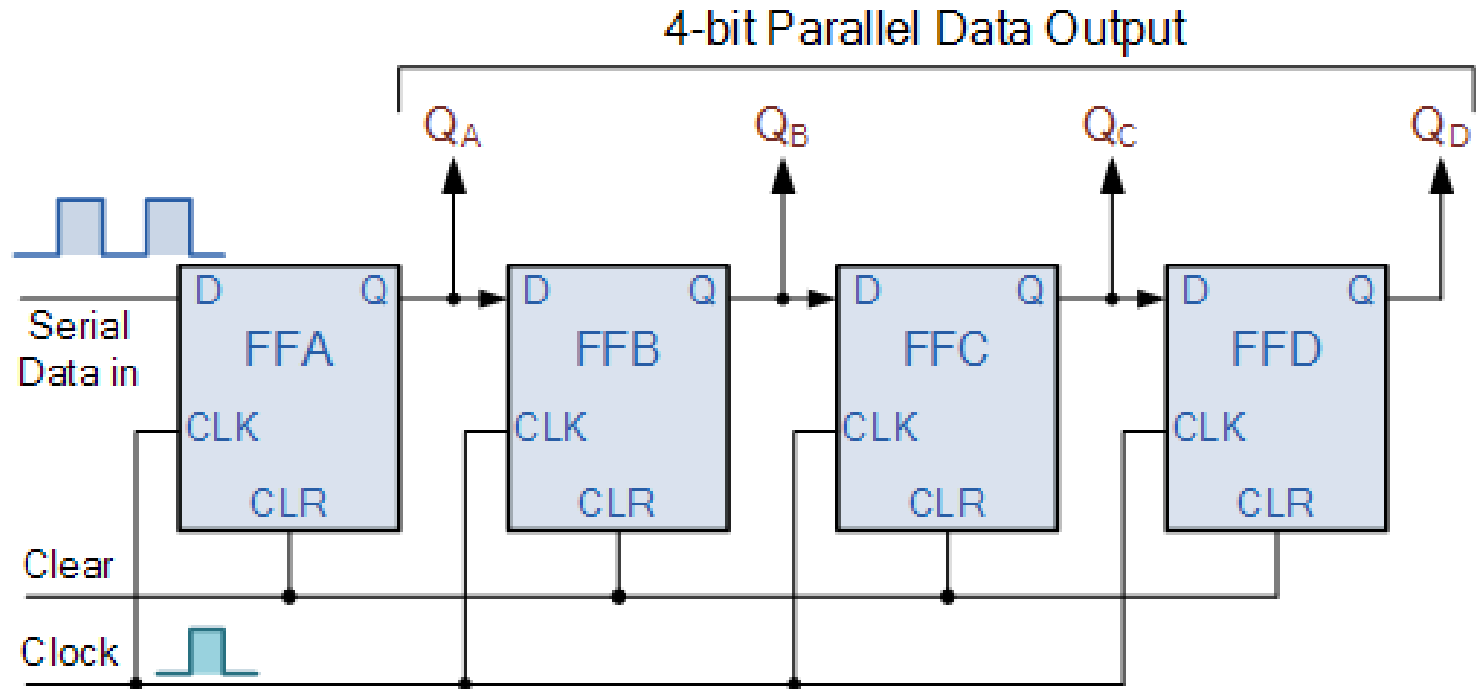
(b) Timing diagram

Serial-in to Parallel-out (SIPO) Shift Register



Serial-in to Parallel-out (SIPO) Shift Register ctd..


Clock Pulse No	Q _A	Q _B	Q _C	Q _D
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	0	0	0	0

 


Recall: Transistor Fabrication

D Transistor fabrication in silicon chips

Traditional Planar Transistor

 


22 nm Tri-Gate Transistor

 

Transistor Implementation of Logic Circuits

 - D Transistors could be used to create simple circuits which implement logic gates.
- D Logic gates are connected together to build simple logic circuits which will perform specific tasks such as:
 - Multiplexers
 - Decoders
 - Flip flops
 - Counters
 - Registers




Microprocessor


D Microprocessor has only a CPU, inside them one or few Integrated Circuits.

D It does not have RAM, ROM and other peripherals.

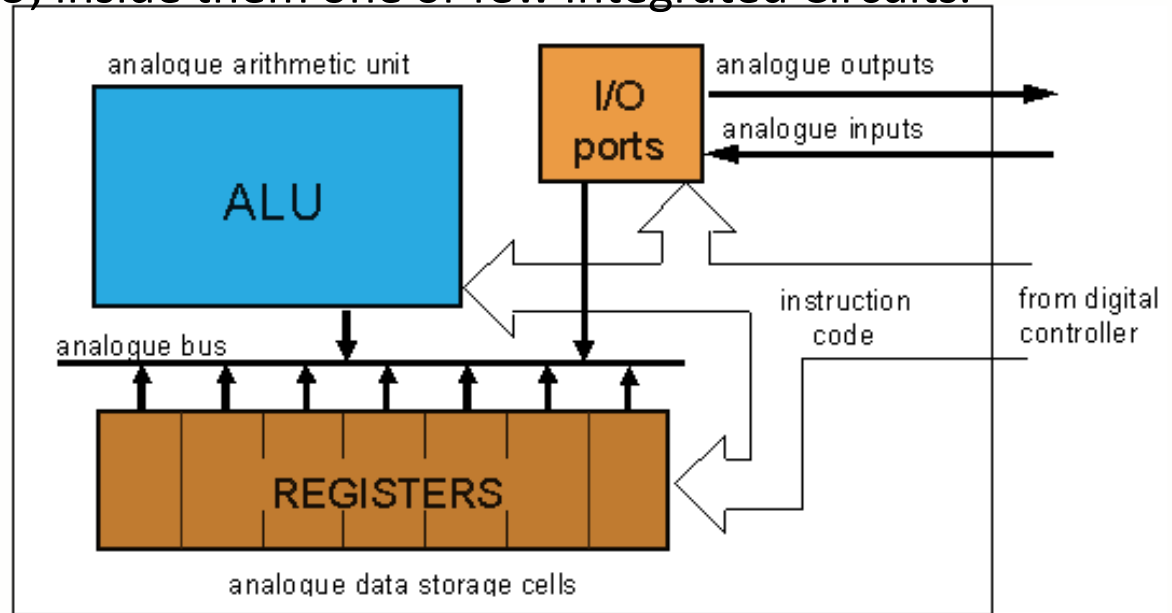
D Microprocessors are not made for specific task but they are required where tasks are complex and tricky



4-bit CPU

 


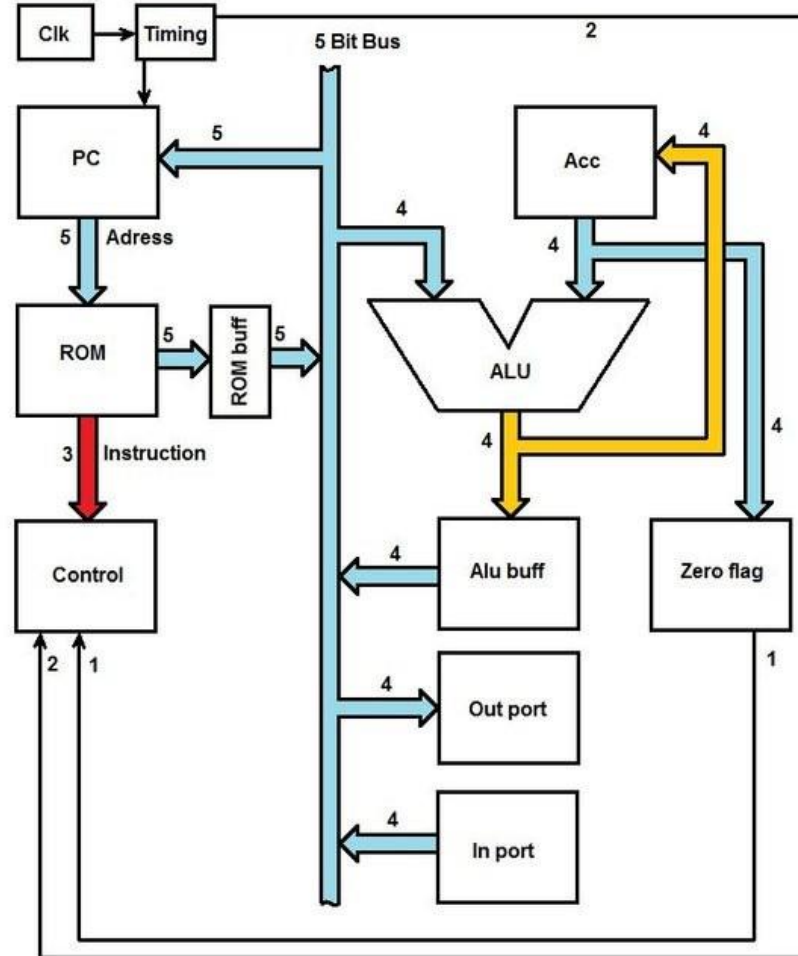
MP-4 CPU Complete diagram by M.K.PEKER 14 May 2017



Processor Manufacturing

FPGA

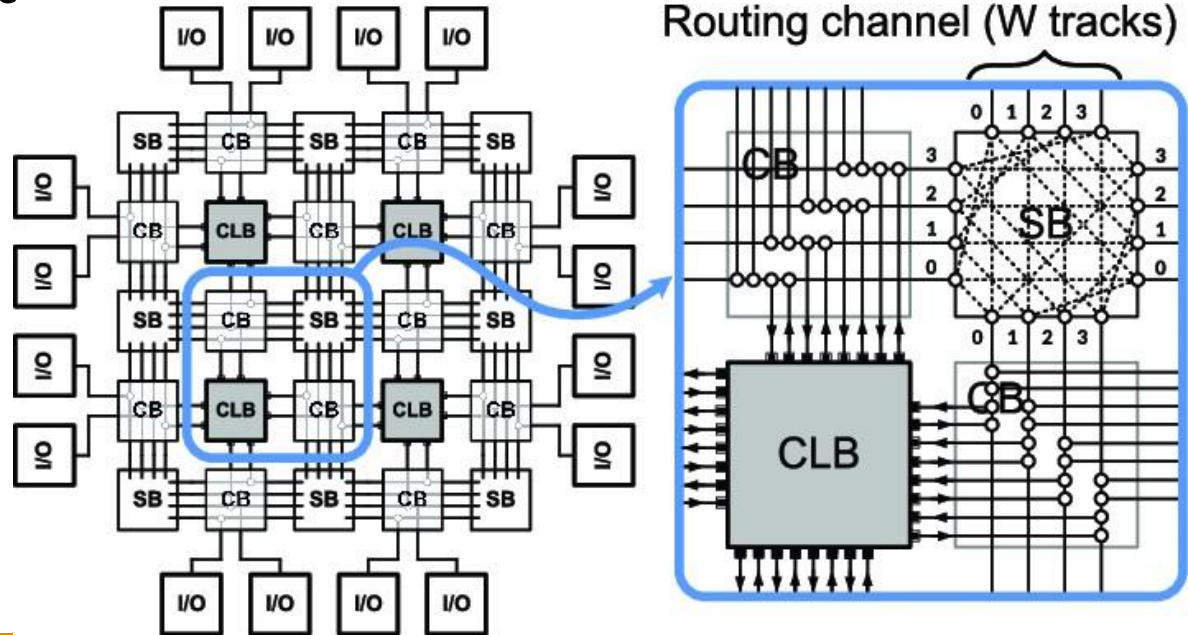 - D An FPGA is an **array of logic gates**, and this array can be **configured in the field**.
- D It consists of a set of **Configurable Logic Blocks** and **Switching Blocks**.



Thank You!
