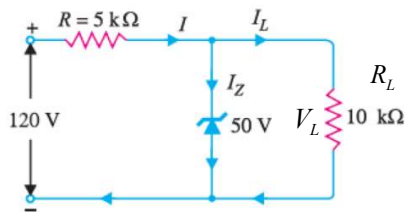




General Sir John Kotelawala Defense University
Basic Electronics
Tutorial 2 – Zener Diodes

Question 1




Find

- (i) the output voltage V_L .
- (ii) the voltage drops across series resistance R
- (iii) the current through Zener diode I_Z .

Solution :

In order to answer this question first we have to check whether the voltage across the Zener diode is greater than 50v.

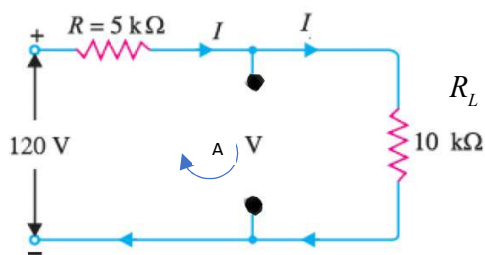Let's find it first. For that let's consider the voltage across the Zener diode as V as shown in the following diagram.



Apply KVL across A,

$$V_s = R \times I + R_L I$$

$$I = \frac{V_s}{R + R_L}$$

Voltage across the load resistor R_L

$$V = R_L \times I$$

$$I = \frac{V}{R_L}$$



General Sir John Kotelawala Defense University

Basic Electronics Tutorial 2 – Zener Diodes

Then,


$$\frac{V}{R_L} = \frac{V_s}{R + R_L}$$

$$V = \frac{V_s R_L}{R + R_L} \rightarrow (1)$$

substituting V_s, R, R_L values

$$V = \frac{120 \times 10 \times 10^3}{5 \times 10^3 + 10 \times 10^3} = 80\text{v}$$

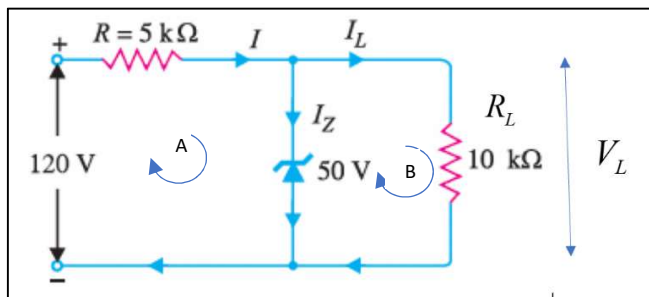The voltage across the Zener diode is more than 50v. Therefore, it is functioning.



Apply KVL across A,

$$120 = 5 \times 10^3 I + 50$$

$$I = 70 / 5 \times 10^3 = 14\text{mA}$$

Voltage across the load resistor R_L is 50v. Where $V_L = 50\text{v}$.

So,

$$50 = R_L \times I_L$$

$$I_L = \frac{50}{10 \times 10^3} = 5\text{mA}$$

Where $I = I_L + I_Z$

$$\text{then, } I_L = 14\text{mA} - 5\text{mA} = 9\text{mA}$$

The voltage across the resistor R V_R is


$$V_R = IR$$

$$V_R = 14 \times 10^{-3} \times 5 \times 10^3 = 60\text{v}$$



General Sir John Kotelawala Defense University
Basic Electronics
Tutorial 2 – Zener Diodes

Question 2

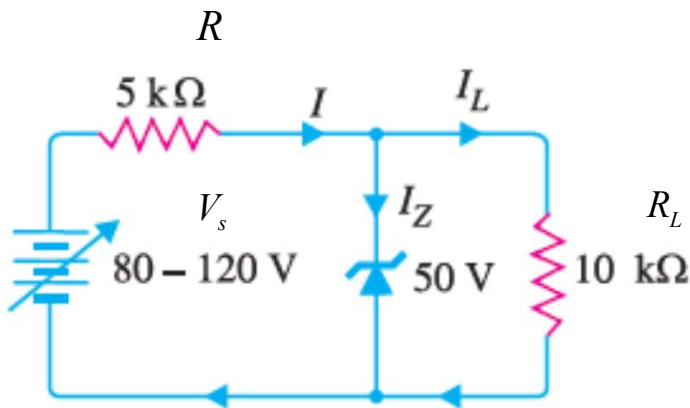

Find the maximum and minimum values of Zener diode current.

Solution :

In this circuit the input voltage range between 80 to 120 v.

This means at 80v input, the circuit has the minimum current flow and at 120v it flows the maximum current.

Firstly, let's check whether the Zener diode is functioning. For that let's check the voltage across the Zener diode similar in Question 1 using equation (1).

Then

$$V = \frac{V_s R_L}{R + R_L} \rightarrow (1)$$

substituting R, R_L values when $V_s = 80\text{v}$

$$V = \frac{80 \times 10 \times 10^3}{5 \times 10^3 + 10 \times 10^3} = 53.33\text{v}$$


substituting R, R_L values when $V_s = 120\text{v}$

$$V = \frac{120 \times 10 \times 10^3}{5 \times 10^3 + 10 \times 10^3} = 80\text{v}$$

The voltage across the Zener diode is more than 50v. Therefore, it is functioning for both minimum and maximum input values.



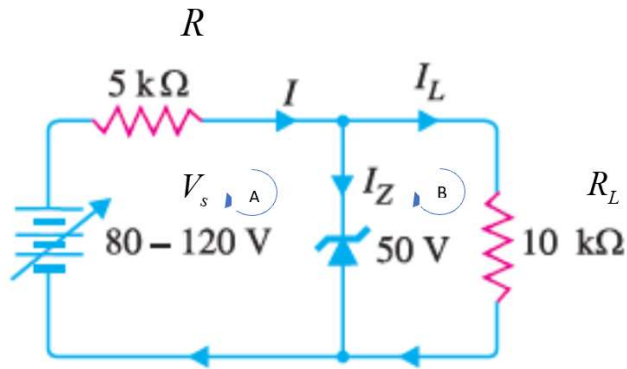General Sir John Kotelawala Defense University
Basic Electronics
Tutorial 2 – Zener Diodes



When $V_s = 80\text{v}$,
apply KVL across A
 $80\text{v} = 5 \times 10^3 \times I + 50\text{v}$
 $I = 6\text{mA}$
apply KVL across B
 $50 = 10 \times 10^3 \times I_L$
 $I_L = 5\text{mA}$
So $I_z (\text{min}) = I - I_L = 1\text{mA}$


When $V_s = 120\text{v}$,
apply KVL across A
 $120\text{v} = 5 \times 10^3 \times I + 50\text{v}$
 $I = 14\text{mA}$
apply KVL across B
 $50 = 10 \times 10^3 \times I_L$
 $I_L = 5\text{mA}$
So $I_z (\text{max}) = I - I_L = 9\text{mA}$



General Sir John Kotelawala Defense University
Basic Electronics
Tutorial 2 – Zener Diodes

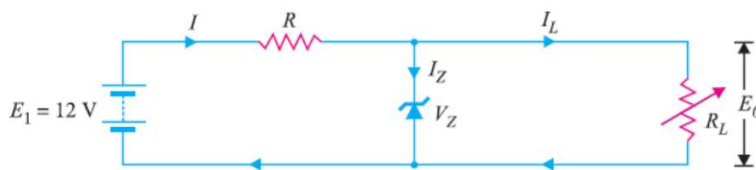Question 3

A 7.2 V Zener ($V_Z = 7.2\text{V}$) is used in the circuit shown in below and the load current (I_L) is to vary from 12 to 100 mA. Find the value of series resistance R to maintain a voltage of 7.2 V across the load (R_L). The input voltage is constant at 12V and the minimum Zener current is 10 mA.



Solution :

In this circuit the input voltage is 12 v and current across the load (I_L) is between 12 mA and 100 mA.

When the minimum Zener current of 10mA flows through the Zener diode the maximum load current of 100mA flows across the load.

Therefore,

$$E_1 = IR + V_Z \rightarrow (1)$$

where $I = I_L + I_Z$

$$I = 100 \times 10^{-3} + 10 \times 10^{-3} = 110 \text{ mA}$$

substituting I, E_1, V_Z values in (1) then


$$R = \frac{12 - 7.2}{110 \times 10^{-3}} = 43.63 \Omega$$



General Sir John Kotelawala Defense University
Basic Electronics
Tutorial 2 – Zener Diodes

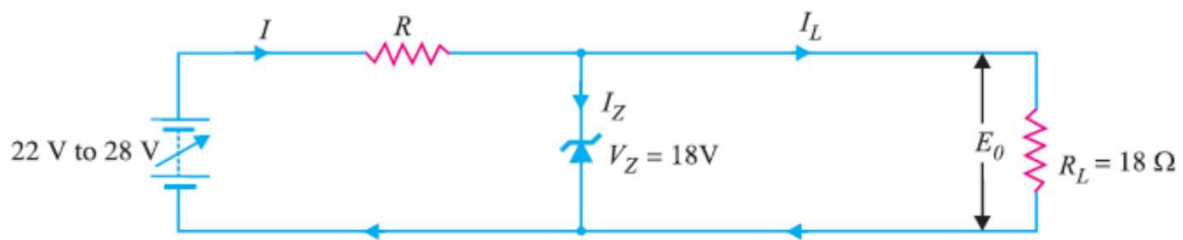Question 4

The voltage across the load stays at 18 V as long as I_Z is maintained between 200 mA and 2 A with a Zener diode where $V_Z = 18$ V. Find the value of series resistance R so that E_0 remains 18V while input voltage E_i is free to vary between 22 V to 28V.



Solution :

In this circuit the input voltage is between 22 V and 28V and current across the Zener diode I_Z is 200 mA and 2 A.

The Zener current will be minimum (i.e. 200 mA) when the input voltage is minimum (i.e. 22 V).

$$\text{Where } V_Z = I_L R_L$$

$$I_L = \frac{18}{18} = 1A$$

$$\text{Also } I = I_L + I_Z$$

$$I = 1 + 0.2 = 1.2A$$

Further,

$$E_i = IR + V_Z$$

$$22 = 1.2R + 18$$

$$R = 3.3\Omega$$