


## (f) Distortion Minimization PWM

This PWM has some similarities with the harmonic elimination PWM. (HEM) (HEP)

- In HEM, we remove a selected set of harmonics from the output voltage. In distortion minimization PWM we minimize the total harmonic distortion due to all harmonics upto a selected upper order in the output voltage.

For most practical applications the dist. min. PWM works better than the HEP.

### (i) 1-phase PWM

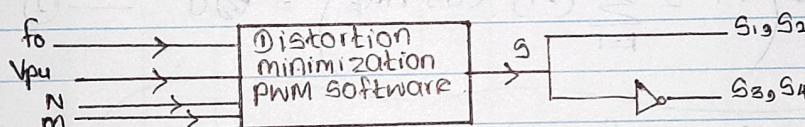


$f_0$  = Fund. frequency of  $V_{o_0}$  required.

$V_{pu}$  = Magnitude of  $V_{o_0}$  required.

$N$  = Upper harmonic minimization order of harmonics included in the harmonic minimization.

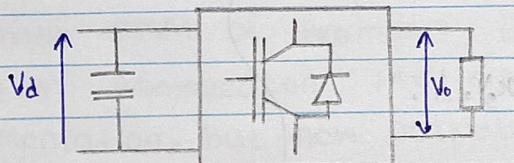$m$  = no. of switching points per quarter cycle of  $V_o$ , chosen.



$$V_o = \sum b_n \sin(n\omega t)$$

$$b_n = \begin{cases} \frac{4V_d}{n\pi} \left( 1 + 2 \sum_{k=1}^m (-1)^k \cos(kx_F) \right); & \text{for EVEN } m \\ -\frac{4V_d}{n\pi} \left( 1 + 2 \sum_{k=1}^m (-1)^k \cos(kx_F) \right); & \text{for ODD } m \end{cases}$$

Total rms value of harmonics up to  $N^{\text{th}}$  order,

$$V_{\text{harmonics}} = \sqrt{\sum_{n=3}^N \left( \frac{b_n}{\sqrt{2}} \right)^2}$$

$$V_{\text{harmonics}} = \sqrt{\sum_{n=3}^N \frac{1}{2} \left( \frac{4V_d}{n\pi} \left( 1 + 2 \sum_{k=1}^m (-1)^k \cos n\alpha_k \right) \right)^2} \quad \text{--- (1)}$$

Considering the fundamental component,

$$V_{\text{pu}} \cdot \left( \frac{4V_d}{\pi} \right) = b_1 = \frac{4V_d}{\pi} \left( 1 + 2 \sum_{k=1}^m (-1)^k \cos n\alpha_k \right);$$

(+ for even m.  
- for odd m.)

$$\therefore V_{\text{pu}} = \pm \left( 1 + 2 \sum_{k=1}^m (-1)^k \cos n\alpha_k \right) = \pm 0 \quad \text{--- (2)}$$

$Z = f(x, y)$  ← function to be minimized  
 $g(x, y) = 0$  ← constraint.

How do we get  $\underline{Z}_{\min}$ ?

$$F = f(x, y) + \lambda g(x, y)$$

$$\frac{\partial F}{\partial x} = 0 \quad \text{--- (1)}$$

$$\frac{\partial F}{\partial y} = 0 \quad \text{--- (2)}$$

$$\frac{\partial F}{\partial \lambda} = 0 \quad \text{--- (3)}$$

$x, y, \lambda$

Equation ① is the function to be minimized, e.g.

Equation ② is the constraint.

Using standard mathematical software, we can find  $\alpha_1, \alpha_2, \alpha_3, \dots, \alpha_m$  and  $\alpha_k$  that make Vharmonic minimum.


We repeat these calculations for different m and N combinations, and store  $\alpha_1, \alpha_2, \dots, \alpha_m$  data in lookup tables.


Vpu	$\alpha_1$	$\alpha_2$	$\alpha_3$	...	$\alpha_m$	
0.00	✓	✓	✓	...	✓	
0.05	✓	✓	✓	...	✓	
0.10	✓	✓	✓	...	✓	
:	:	:	:	..	..	
:	:	:	:	..	..	
0.95	✓	✓	-	..	✓	Lookup table for one set of
1.00	✓	-	✓	..	✓	m and N.

Therefore, the implementation of the PHIM is same as that of the Harmonic Elimination PWM.

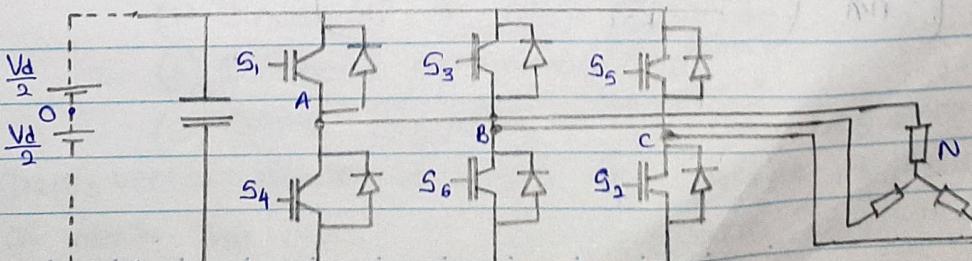
### Note

3-phase PWM of harmonic Elimination PHIM and Distortion Minimization PWM are similar to their 1-phase implementation, but now output three switching signals  $S_A, S_B$  and  $S_C$ . In fact  $S_B$  and  $S_C$  are deduced from  $S_A$ , according to 3-phase symmetry.



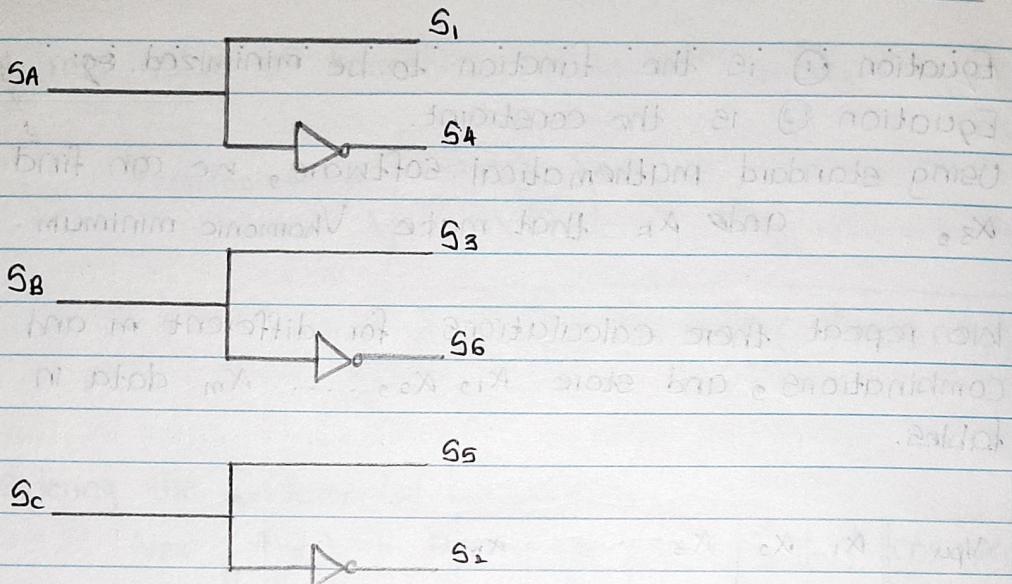

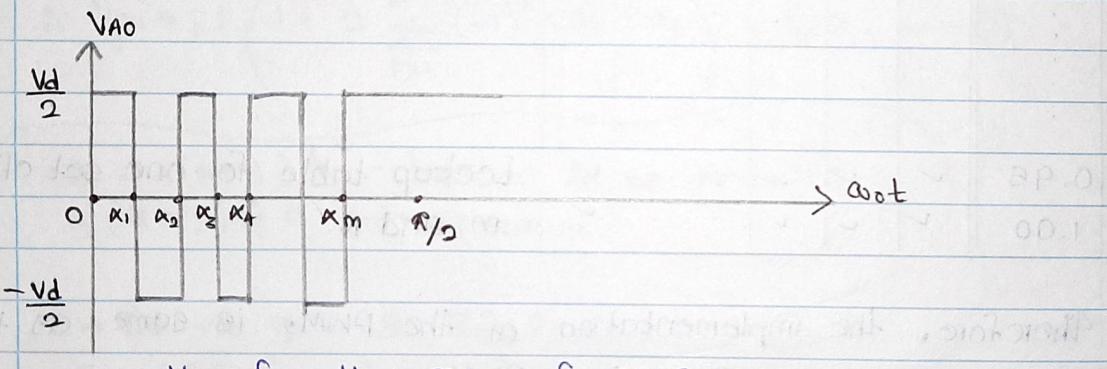It is the pole-voltage  $V_{AO}$  that represents switching signal  $S_A$  in the 3ph. inverter.



$V_{AO}$  for the case of an EVEN number of phases.

$$V_{AO} = \sum_{n=1,3,5} b_n \sin(n\omega t)$$

$$b_n = \begin{cases} \frac{2V_d}{n\pi} \left( 1 + 2 \sum_{k=1}^m (-1)^k \cos n\alpha_k \right); & \text{for EVEN } m \\ -\frac{2V_d}{n\pi} \left( 1 + 2 \sum_{k=1}^m (-1)^k \cos n\alpha_k \right); & \text{for ODD } m \end{cases}$$

1ph: 5 nos harm  
 3rd, 5th, 7th, 9th, 11th  
 3ph: 5 nos  
 5th, 7th, 11th, 13th, 17th

We must use this bn expressions when computing  $\alpha_1, \alpha_2 \dots$  and  $\alpha_m$  for SA of a 3-phase inverter.

Another important difference is the orders of harmonics to be eliminated (or to be considered for minimization). The 3ph. inverter does not produce triplen order harmonics (i.e., 3, 9, 15, 21 ...) in the output voltage, so we do not need to consider these.

eg: If we want to remove 5 nos of harmonics in the harmonic elimination PWM, then we select,

1-phase: 3rd, 5th, 7th, 9th, 11th

3-phase: 5th, 7th, 11th, 13th and 17th

If we want to minimize harmonics up to Nth order in the distortion minimization PWM, then,

$$\text{1-phase: } V_{\text{harmonics}} = \sqrt{\sum_{n=1,3,5}^N \left(\frac{b_n}{V_2}\right)^2}$$

$$\text{3-phase: } V_{\text{harmonic}} = \sqrt{\sum_{n=5,7,11,\dots}^N \left(\frac{b_n}{V_2}\right)^2}$$

### (g) Voltage Vector PWM.

"Vector" is a mathematical tool used to model 3 phase quantities, such as voltage, current, magnetic flux, etc. The speciality of vector is that it handles any 3 ph. variation, irrespective of whether it is,

- (i) Sinusoidal or non sinusoidal.
- (ii) Balanced or unbalanced.
- (iii) Some frequency or different frequencies.

Thus, vector is an ideal tool to analyse 3 phase inverters, of which the output is non-sinusoidal (i.e pulsed output).

### (i) Definition

$V_a(t)$  = instantaneous voltage of phase - a

$V_b(t)$  = instantaneous voltage of phase - b

$V_c(t)$  = instantaneous voltage of phase - c

Voltage vector  $\bar{V}(t)$  is defined as,

$$\bar{V}(t) = V_a(t) + \alpha \{V_b(t) + \alpha^2 V_c(t)\}$$

$$\alpha = 1/\sqrt{2}^\circ$$

$$= \cos 120^\circ + j \sin 120^\circ$$

For vector definition to hold, the summation

$$V_a(t) + V_b(t) + V_c(t) \text{ must be zero for all } t.$$

Real part of a vector is called  $\alpha$ -component

Imaginary part of a vector is called  $\beta$ -component.

Ex: At an instant of time, the voltages of phases a, b and c are given as 420V, -100V, and -320V, respectively. Find the magnitude and the direction of voltage vector of this instant. Show your result on an  $\alpha$ - $\beta$  plane.

Ans:

$$V_a = 420V$$

$$V_b = -100V$$


$$V_c = -320V$$

$$\bar{V} = V_a + \alpha V_b + \alpha^2 V_c$$

$$= 420 + (1/\sqrt{2}^\circ)(-100) + (1/\sqrt{2}^\circ)^2(-320)$$

$$= 420 - 100\sqrt{2}^\circ - 320\sqrt{2}^\circ$$

$$= 718.6 \angle 21.2^\circ V$$

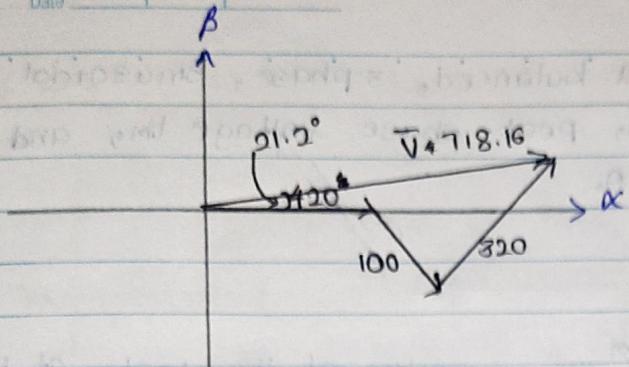

## (2) Voltage vector for a balanced, 3-phase, sinusoidal voltage.

$$V_a = V_m \cos(\omega t + \theta_0)$$

$$V_b = V_m \cos(\omega t + \theta_0 - 120^\circ)$$

$$V_c = V_m \cos(\omega t + \theta_0 - 240^\circ); \theta_0 \text{ is same initial phase angle.}$$

$$\bar{V} = (V_m \cos(\omega t + \theta_0)) + (1/\sqrt{2}) (V_m \cos(\omega t + \theta_0 - 120^\circ)) + (1/\sqrt{2}) (V_m \cos(\omega t + \theta_0 - 240^\circ)).$$

$$= V_m \cos(\omega t + \theta_0) + (\cos 120^\circ + j \sin 120^\circ) V_m \cos(\omega t + \theta_0 - 120^\circ) + (\cos 240^\circ + j \sin 240^\circ) V_m \cos(\omega t + \theta_0 - 240^\circ)$$

$$= V_m (\cos(\omega t + \theta_0) + \cos 120^\circ \cos(\omega t + \theta_0 - 120^\circ) + \cos 240^\circ \cdot \cancel{\cos(\omega t + \theta_0 - 240^\circ)}) + j V_m (\sin 120^\circ \cos(\omega t + \theta_0 - 120^\circ) + \sin 240^\circ \cdot \cos(\omega t + \theta_0 - 240^\circ)).$$

$$= \frac{V_m}{2} \left( 3 \cos(\omega t + \theta_0) + [\cos(\omega t + \theta_0 - 120^\circ) + \cos(\omega t + \theta_0 - 240^\circ)] \right) +$$

$$j \frac{V_m}{2} \left( 3 \sin(\omega t + \theta_0) - [\sin(\omega t + \theta_0) + \sin(\omega t + \theta_0 - 120^\circ) + \sin(\omega t + \theta_0 - 240^\circ)] \right).$$


$$= \frac{3V_m}{2} [\cos(\omega t + \theta_0) + j \sin(\omega t + \theta_0)] //$$

$$= \frac{3V_m}{2} (\omega t + \theta_0).$$

$$\bar{V} = \frac{3}{2} V_m \angle \omega t + \theta_0 = \frac{3}{2} V_m [\cos(\omega t + \theta_0) + j \sin(\omega t + \theta_0)].$$

Voltage vector for a balanced 3-phase sinusoidal voltage of ang. fr.  $\omega$ ,

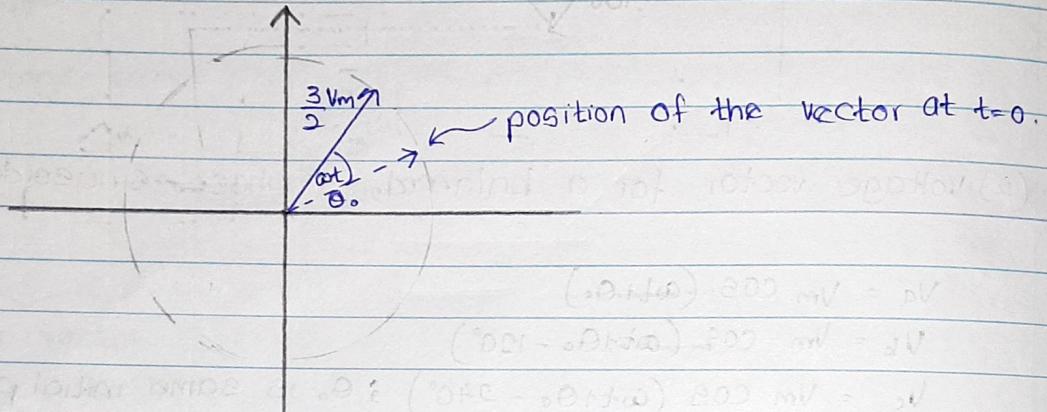Voltage vector for a balanced, 3 phase, sinusoidal voltage of ang. frequency  $\omega$ , peak-phase voltage  $V_m$ , and initial phase angle  $\theta_0$ .



This shows us that the voltage vector for a balanced, 3ph. sinusoidal voltages rotate at uniform angular velocity at  $\omega$  in CCW direction with a constant amplitude of  $3/2 V_m$ .

$$Ex: V_a = V_m \sin(\omega t + \theta_0) \text{ and } (0.866) 300 \text{ mV} = 200 \text{ mV}$$

$$V_b = V_m \sin(\omega t - 120^\circ) = 0.5 \cdot 300 = 150 \text{ mV}$$

$$V_c = V_m \sin(\omega t - 240^\circ) = 0.5 \cdot 300 = 150 \text{ mV}$$


Illustrate  $\bar{V}$  on  $\alpha, \beta$  plane.

$$Ans: (0.866) 300 + (0.5 - 0.866) 300 + (0.5 + 0.866) 300 \text{ mV} =$$



$$V_a = V_m \sin \omega t = V_m \cos(\omega t - 90^\circ)$$

$$V_b = V_m \cos(\omega t - 90^\circ - 120^\circ) = 0.5 \cdot 300 = 150 \text{ mV}$$
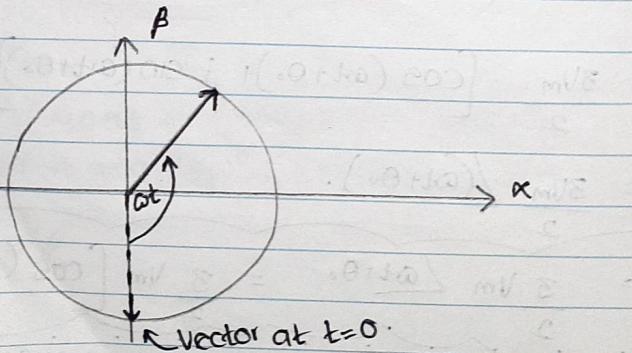
$$V_c = V_m \cos(\omega t - 90^\circ - 240^\circ) = 0.5 \cdot 300 = 150 \text{ mV}$$


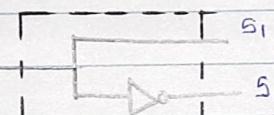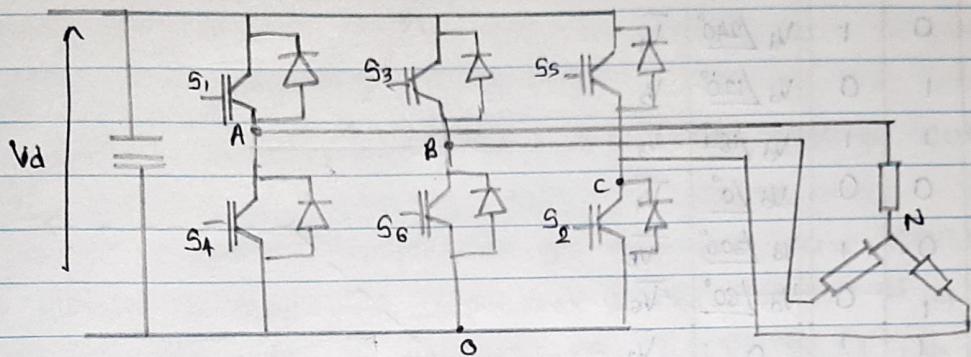
### (3) Voltage vectors produced 3ph. Inverter.




output phase voltages:

$$V_{AN}, V_{BN}, V_{CN}$$



$$S_3$$

$$S_6$$

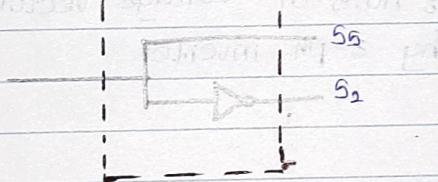

$$S_5$$

$$S_2$$

$$\bar{V} = V_{AN} + \underline{\alpha} V_{BN} + \underline{\alpha^2} V_{CN}$$

$$= (V_{AO} - V_{NO}) + \underline{\alpha} (V_{BO} - V_{NO}) + \underline{\alpha^2} (V_{CO} - V_{NO})$$

$$= V_{AO} + \underline{\alpha} V_{BO} + \underline{\alpha^2} V_{CO} - \underbrace{(1 + \underline{\alpha} + \underline{\alpha^2})}_{0} V_{NO}$$

$$= V_{AO} + \underline{\alpha} V_{BO} + \underline{\alpha^2} V_{CO}$$

$$V_{AO} = S_A V_d$$

$$V_{BO} = S_B V_d$$

$$V_{CO} = S_C V_d$$

$$\bar{V} = S_A V_d + \underline{\alpha} (S_B V_d) + \underline{\alpha^2} (S_C V_d)$$

$$= (S_A + \underline{\alpha} S_B + \underline{\alpha^2} S_C) V_d$$

$S_A$	$S_B$	$S_C$	$\bar{V}$
0	0	0	0
0	0	1	$V_d / 240^\circ$
0	1	0	$V_d / 120^\circ$
0	1	1	$V_d / 180^\circ$
1	0	0	$V_d / 0^\circ$
1	0	1	$V_d / 300^\circ$
1	1	0	$V_d / 60^\circ$
1	1	1	0

For set B output

$V_0$   $V_6$

$V_2$   $V_4$

$V_5$   $V_1$

$V_3$   $V_7$

$V_6$   $V_0$

$V_4$   $V_2$

$V_1$   $V_5$

$V_7$   $V_3$

$V_0$   $V_6$

$V_2$   $V_4$

$V_5$   $V_1$

$V_3$   $V_7$

$V_6$   $V_0$

$V_4$   $V_2$

$V_1$   $V_5$

$V_7$   $V_3$

$V_0$   $V_6$

$V_2$   $V_4$

$V_5$   $V_1$

$V_3$   $V_7$

$V_6$   $V_0$

$V_4$   $V_2$

$V_1$   $V_5$

$V_7$   $V_3$

$V_0$   $V_6$

$V_2$   $V_4$

$V_5$   $V_1$

$V_3$   $V_7$

$V_6$   $V_0$

$V_4$   $V_2$

$V_1$   $V_5$

$V_7$   $V_3$

$V_0$   $V_6$

$V_2$   $V_4$

$V_5$   $V_1$