



# Gates and Combinational Logic Design


---

LECTURE 12

DR. SK WIJAYASEKARA

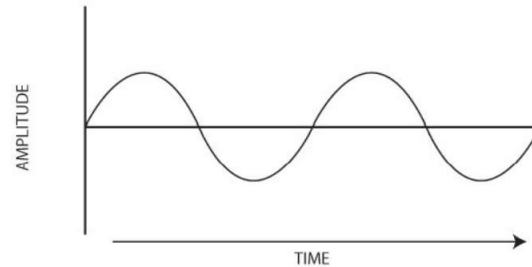
## Analog Signals

- ▢ Continuously changing signals
- ▢ Signal values at different times are useful information



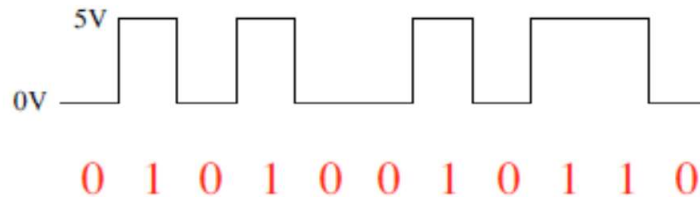
## Digital Signals

- ▢ Assumes just a few analog values. e.g., 0V and 5V
- ▢ Transmit information in the form of a sequence of 0V and 5V segments



# Gates and Logic Design

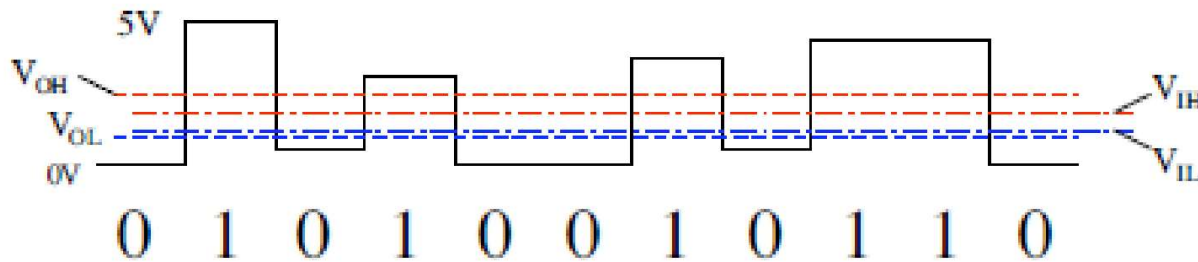**Generation:**

Any voltage higher than  $V_{OH}$  is HIGH. ( $V_{OH} = 2.4V^*$ )

Any voltage lower than  $V_{OL}$  is LOW. ( $V_{OL} = 0.4V$ )

**Detection:**

Any voltage higher than  $V_{IH}$  is HIGH. ( $V_{IH} = 2.0V$ )

Any voltage lower than  $V_{IL}$  is LOW. ( $V_{IL} = 0.8V$ )

# Digital Signals

$X$	$Y$	$Z$
0	0	0
0	1	0
1	0	0
1	1	1

Truth table of **AND**



$X$	$Y$	$Z$
0	0	0
0	1	1
1	0	1
1	1	1

Truth table of **OR**



$X$	$Z$
0	1
1	0

Truth table of **NOT**



$X$	$Y$	$Z$
0	0	1
0	1	1
1	0	1
1	1	0

Truth table of **NAND**



$X$	$Y$	$Z$
0	0	1
0	1	0
1	0	0
1	1	0

Truth table of **NOR**



$X$	$Y$	$Z$
0	0	0
0	1	1
1	0	1
1	1	0

Truth table of **XOR** (Exclusive OR)




# Truth Tables

$X$	$Y$	$Z$
0	0	0
0	1	0
1	0	0
1	1	1

Truth table of AND


$$Z = X.Y$$

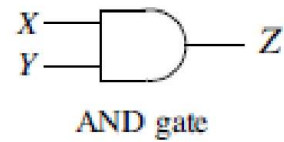

$X$	$Y$	$Z$
0	0	1
0	1	1
1	0	1
1	1	0

Truth table of NAND

$$Z = \overline{X.Y}$$

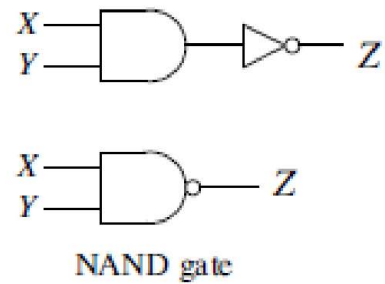


# Boolean Algebra

$X$	$Y$	$Z$
0	0	0
0	1	1
1	0	1
1	1	1

Truth table of OR



$$Z = X + Y$$

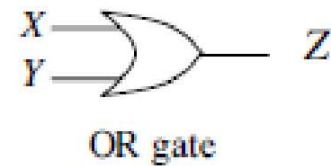

$X$	$Y$	$Z$
0	0	1
0	1	0
1	0	0
1	1	0

Truth table of NOR

$$Z = \overline{X + Y}$$

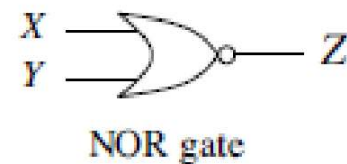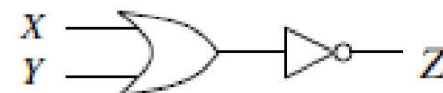

Boolean Algebra

# Boolean Algebra Simplification

---

## Basic Laws

Commutative:  $X+Y = Y+X$   
 $X.Y = Y.X$

Associative:  $X+Y+Z = (X+Y)+Z = X+(Y+Z)$   
 $X.Y.Z = (X.Y).Z = X.(Y.Z)$

Distributive:  $X.(Y+Z) = X.Y + X.Z$

De Morgan's:  $\overline{X+Y} = \overline{X} . \overline{Y}$   
 $\overline{X.Y} = \overline{X} + \overline{Y}$

# Expression from Truth Table

- ❑ Min-term corresponds to the product term that give a 1 in the output
- ❑ Output expression is obtained by adding up all min-terms

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

The expression for Z is

$$Z = \bar{X}.Y + X.\bar{Y} + X.Y$$

- Can be simplified down to  $Z = X + Y$

$$\begin{aligned}
 Z &= \bar{X}.\bar{Y} + \bar{X}.Y + X.\bar{Y} \\
 &= \bar{X}.(\bar{Y} + Y) + X.\bar{Y} \\
 &= \bar{X}.1 + X.\bar{Y} \\
 &= \bar{X} + X.\bar{Y} \\
 &= \overline{(X.(\bar{X} + Y))} \\
 &= \overline{(X.\bar{X} + X.Y)} \\
 &= \overline{X.Y}
 \end{aligned}$$

$$Y + \bar{Y} = 1$$

$$\bar{X}.1 = \bar{X}$$

De Morgan's law

Distributive

$$\bar{X}.X = 0$$



# Expression from Truth Table

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

The expression for Z is

$$Z = \bar{X}.\bar{Y} + \bar{X}.Y + X.\bar{Y}$$

$$\begin{aligned}
 Z &= \bar{X}.\bar{Y} + \bar{X}.Y + X.\bar{Y} \\
 &= \bar{X}.(\bar{Y} + Y) + X.\bar{Y} \\
 &= \bar{X}.1 + X.\bar{Y} \\
 &= \bar{X} + X.\bar{Y} \\
 &= \overline{(X.(\bar{X} + Y))} \\
 &= \overline{(X.\bar{X} + X.Y)} \\
 &= \bar{X}.Y
 \end{aligned}$$

$$Y + \bar{Y} = 1$$

$$\bar{X}.1 = \bar{X}$$

De Morgan's law

Distributive

$$\bar{X}.X = 0$$

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

The expression for Z is

$$Z = \bar{X}.\bar{Y}$$



Truth table of NOR

# Circuit Realization

Example 1.

$$Z = \bar{X}.\bar{Y} + \bar{X}.Y + X.\bar{Y}$$


**Note:** This is same as a NAND gate

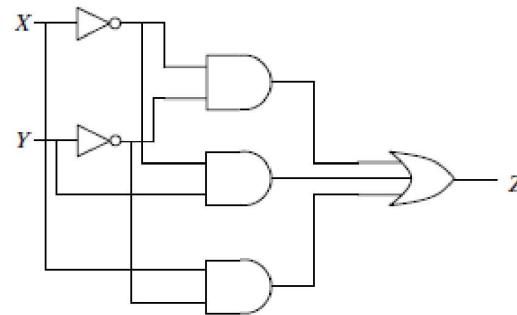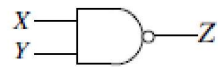

Example 2.

□ Derive the circuit for this combinational logic.

$$x = \bar{a}\bar{c} + b + ac$$

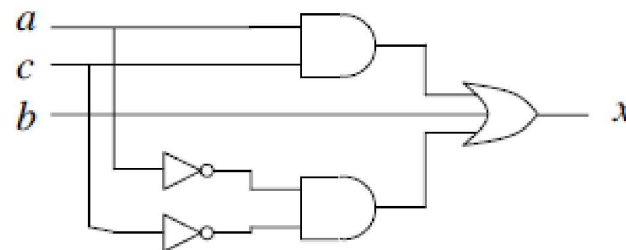

### Example 3.

□ binary code to Gray code conversion

Binary			Gray code		
<i>a</i>	<i>b</i>	<i>c</i>	<i>x</i>	<i>y</i>	<i>z</i>
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	0	1	1	1	1
1	1	0	1	0	1
1	1	1	1	0	0

$$x = \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + a\bar{b}\bar{c} + abc$$

$$y = \bar{a}b\bar{c} + \bar{a}bc + a\bar{b}\bar{c} + a\bar{b}c$$

$$z = \bar{a}b\bar{c} + \bar{a}bc + a\bar{b}c + abc$$

- For each of x, y and z, we need a number of inverters, plus 4 AND gates and a multi-input OR gates

# Karnaugh Maps - Simplification for Two Variables

- The best way of selecting two groups of 1s from our simple Kmap is shown below.
- We see that both groups are powers of two and that the groups overlap.
- The next slide gives guidance for selecting Kmap groups.

		Y	
		0	1
X	0	0	1
	1	1	1

# Kmap Simplification for Two Variables

---

The rules of Kmap simplification are:

- Groupings can contain only 1s; no 0s.
- Groups can be formed only at right angles; diagonal groups are not allowed.
- The number of 1s in a group must be a power of 2 – even if it contains a single 1.
- The groups must be made as large as possible.
- Groups can overlap and wrap around the sides of the Kmap.

# Kmap Simplification for Three Variables

A Kmap for three variables is constructed as shown in the diagram below.

We have placed each minterm in the cell that will hold its value.

- Notice that the values for the yz combination at the top of the matrix form a pattern that is not a normal binary sequence.

x \ yz	yz			
	00	01	11	10
0	$\bar{x}\bar{y}\bar{z}$	$\bar{x}\bar{y}z$	$\bar{x}yz$	$\bar{x}y\bar{z}$
1	$x\bar{y}\bar{z}$	$x\bar{y}z$	$xyz$	$xy\bar{z}$

# Kmap Simplification for Three Variables

---

Thus, the first row of the Kmap contains all minterms where  $x$  has a value of zero.

The first column contains all minterms where  $y$  and  $z$  both have a value of zero.

x \ yz	00	01	11	10
0	$\bar{x}\bar{y}\bar{z}$	$\bar{x}\bar{y}z$	$\bar{x}yz$	$\bar{x}y\bar{z}$
1	$x\bar{y}\bar{z}$	$x\bar{y}z$	$xyz$	$xy\bar{z}$

# Kmap Simplification for Three Variables

---

Consider the function:

$$F(X, Y) = \bar{X}\bar{Y}Z + \bar{X}YZ + X\bar{Y}Z + XYZ$$

Its Kmap is given below.

- What is the largest group of 1s that is a power of 2?

x \ yz	yz			
	00	01	11	10
0	0	1	1	0
1	0	1	1	0



# Kmap Simplification for Three Variables

This grouping tells us that changes in the variables  $x$  and  $y$  have no influence upon the value of the function: They are irrelevant.

This means that the function,

reduces to  $F(x) = z$ .

$$F(X, Y) = \bar{X}\bar{Y}Z + \bar{X}YZ + X\bar{Y}Z + XYZ$$

**You could verify  
this reduction  
with identities or  
a truth table.**

X \ YZ	YZ			
	00	01	11	10
0	0	1	1	0
1	0	1	1	0

# Kmap Simplification for Three Variables

Now for a more complicated Kmap. Consider the function:

$$F(X, Y, Z) = \bar{X}\bar{Y}\bar{Z} + \bar{X}\bar{Y}Z + \bar{X}YZ + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XY\bar{Z}$$

Its Kmap is shown below. There are (only) two groupings of 1s.

- Can you find them?

X \ YZ	YZ			
	00	01	11	10
0	1	1	1	1
1	1	0	0	1

# Kmap Simplification for Three Variables

In this Kmap, we see an example of a group that wraps around the sides of a Kmap.

This group tells us that the values of  $x$  and  $y$  are not relevant to the term of the function that is encompassed by the group.

- What does this tell us about this term of the function?

**What about the green group in the top row?**

x \ yz	yz			
	00	01	11	10
0	1	1	1	1
1	1	0	0	1

# Kmap Simplification for Three Variables

The green group in the top row tells us that only the value of  $x$  is significant in that group.

We see that it is complemented in that row, so the other term of the reduced function is  $\overline{x}$ .

Our reduced function is:  $F(X, Y, Z) = \overline{x} + \overline{z}$

**Recall that we had  
six minterms in our  
original function!**

x \ yz	yz			
	00	01	11	10
0	1	1	1	1
1	1	0	0	1

# Kmap Simplification for Four Variables

Our model can be extended to accommodate the 16 minterms that are produced by a four-input function. This is the format for a 16-minterm Kmap.

WX \ YZ	YZ			
	00	01	11	10
00	$\bar{W}\bar{X}\bar{Y}\bar{Z}$	$\bar{W}\bar{X}\bar{Y}Z$	$\bar{W}\bar{X}Y\bar{Z}$	$\bar{W}\bar{X}YZ$
01	$\bar{W}X\bar{Y}\bar{Z}$	$\bar{W}X\bar{Y}Z$	$\bar{W}XY\bar{Z}$	$\bar{W}XYZ$
11	$WX\bar{Y}\bar{Z}$	$WX\bar{Y}Z$	$WXY\bar{Z}$	$WXYZ$
10	$W\bar{X}\bar{Y}\bar{Z}$	$W\bar{X}\bar{Y}Z$	$W\bar{X}Y\bar{Z}$	$W\bar{X}YZ$

# Kmap Simplification for Four Variables

We have populated the Kmap shown below with the nonzero minterms from the function:

$$F(W, X, Y, Z) = \bar{W}\bar{X}\bar{Y}\bar{Z} + \bar{W}\bar{X}\bar{Y}Z + \bar{W}\bar{X}Y\bar{Z} \\ + \bar{W}XY\bar{Z} + W\bar{X}\bar{Y}\bar{Z} + W\bar{X}\bar{Y}Z + W\bar{X}Y\bar{Z} + W\bar{X}YZ$$

- Can you identify (only) three groups in this Kmap?

**Recall that groups can overlap.**

WX \ YZ	YZ			
	00	01	11	10
00	1	1		1
01				1
11				
10	1	1		1


# Kmap Simplification for Four Variables

Our three groups consist of:

- A purple group entirely within the Kmap at the right.
- A pink group that wraps the top and bottom.
- A green group that spans the corners.

Thus, we have three terms in our final function:
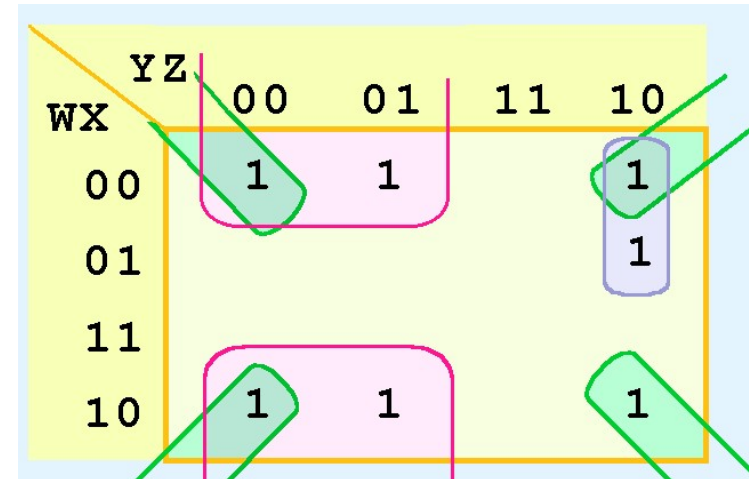
$$F(W, X, Y, Z) = \bar{W}\bar{Y} + \bar{X}\bar{Z} + \bar{W}Y\bar{Z}$$



# Kmap Simplification for Four Variables

It is possible to have a choice as to how to pick groups within a Kmap, while keeping the groups as large as possible.

The (different) functions that result from the groupings below are logically equivalent.

		YZ			
		00	01	11	10
WX	00	1		1	
	01	1		1	1
	11	1			
	10	1			

		YZ			
		00	01	11	10
WX	00	1		1	
	01	1		1	1
	11	1			
	10	1			



# Don't Care Conditions

---

Real circuits don't always need to have an output defined for every possible input.

- For example, some calculator displays consist of 7-segment LEDs. These LEDs can display  $2^7 - 1$  patterns, but only ten of them are useful.

If a circuit is designed so that a particular set of inputs can never happen, we call this set of inputs a *don't care* condition.

They are very helpful to us in Kmap circuit simplification.

# Don't Care Conditions

In a Kmap, a don't care condition is identified by an  $X$  in the cell of the minterm(s) for the don't care inputs, as shown below.

In performing the simplification, we are free to include or ignore the  $X$ 's when creating our groups.

WX \ YZ	YZ			
	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	

# Don't Care Conditions

In one grouping in the Kmap below, we have the function:

$$F(W, X, Y, Z) = \bar{W}\bar{Y} + YZ$$

WX \ YZ	YZ			
	00	01	11	10
00	X	1	1	X
01		X	1	
11	X		1	
10			1	


# Combinational Logic Design

## 1. Single Bit Comparator

$A > B$ ,  $A = B$ ,  $A < B$

Inputs		Outputs		
B	A	A>B	A=B	A<B
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

Truth Table

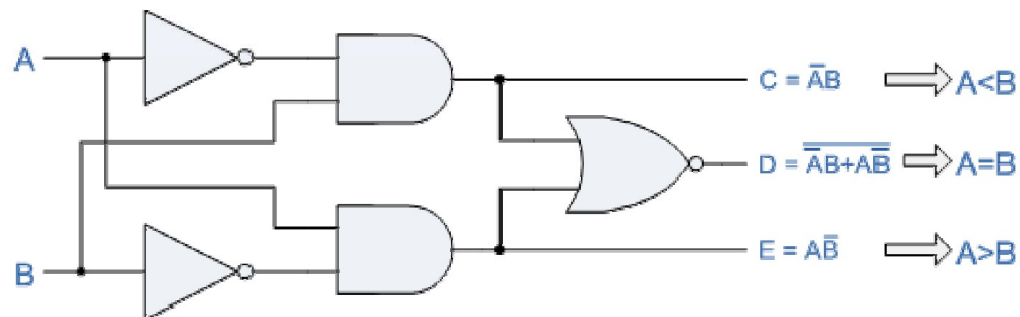

# Combinational Circuits

## Two Bit Comparator

Simplify the minterm expressions to:

$$G = A1 \bullet \overline{B1} + A0 \bullet \overline{B0} \bullet (\overline{B1} + A1)$$

$$E = \overline{(A1 \oplus B1) + (A0 \oplus B0)}$$

$$L = \overline{A0} \bullet B0 \bullet (\overline{A1} + B1) + \overline{A1} \bullet B1$$


Inputs				Outputs		
B[1]	B[0]	A[1]	A[0]	A>B	A=B	A<B
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

# Combinational Circuits – Half Adder

- A half adder adds two one-bit binary numbers  $A$  and  $B$
- It has two outputs, *Sum* and *Carry*

Inputs		Outputs	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Truth Table

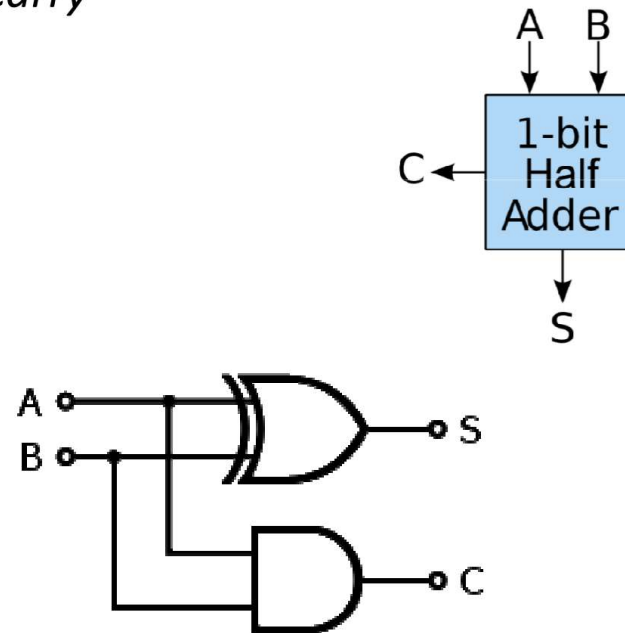

# Combinational Circuits – Full Adder


- A full adder adds binary numbers and carried in value
- A one-bit full adder adds three one-bit numbers,  $A$ ,  $B$ , and  $C_{in}$
- $A$  and  $B$  are the operands, and  $C_{in}$  is a bit carried in

Inputs			Outputs	
A	B	Ci	Co	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Truth Table


$$C_{out} = (A \cdot B) + (C_{in} \cdot (A \oplus B))$$

$$S = A \oplus B \oplus C_{in}$$

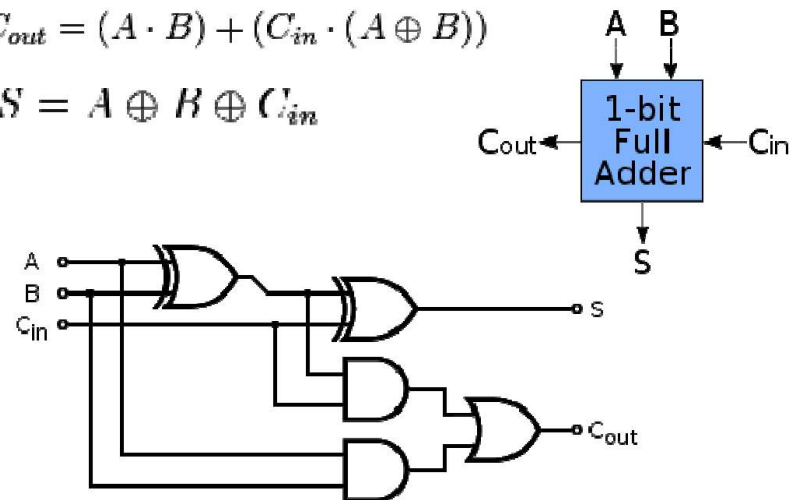

# Combinational Circuits

## 4bit Full Adder

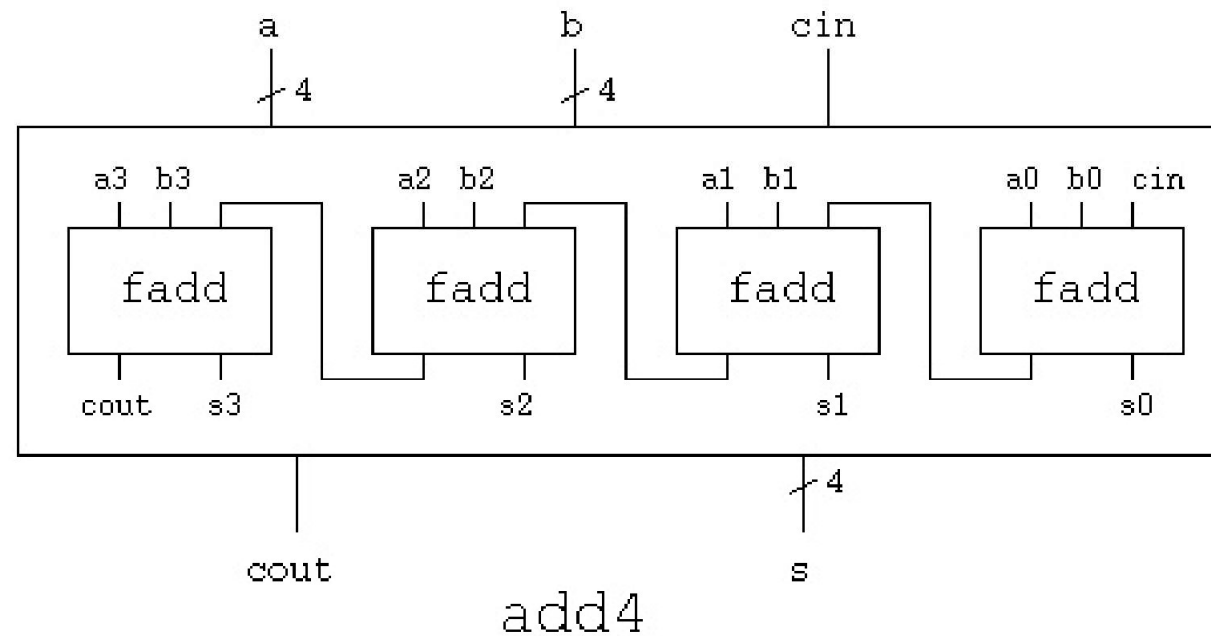



---

# Thank You