




General Sir John Kotelawala Defense University
Basic Electronics
Tutorial 1

Diode Circuit


Diode Approximation:

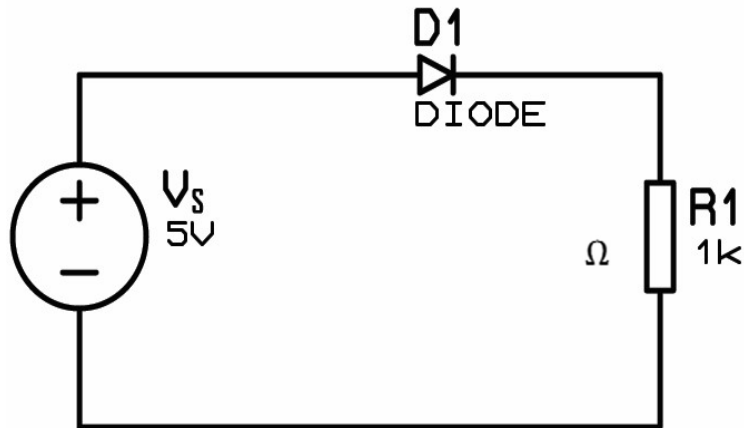1. Let's assume the diode resistance is negligible.



- a. Assume the diode is silicon and find the current across the circuit.
- b. If the $V_s = 0.5V$ find the current across the circuit when,
 - the diode is Germanium
 - the diode is Silicon

2. Find the current across the circuit

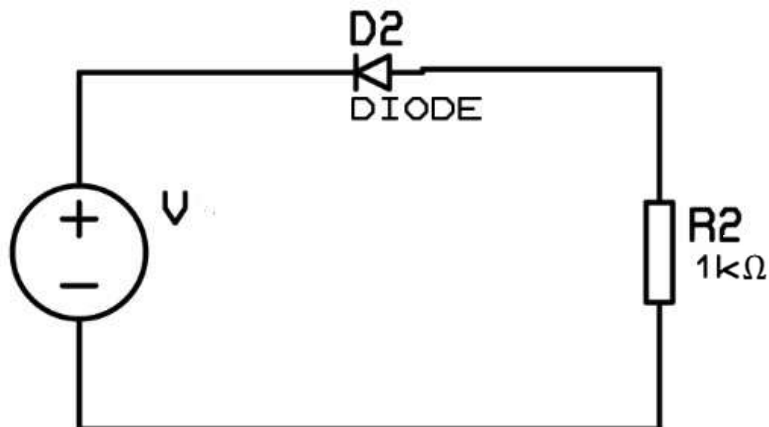




General Sir John Kotelawala Defense University


Basic Electronics

Tutorial 1

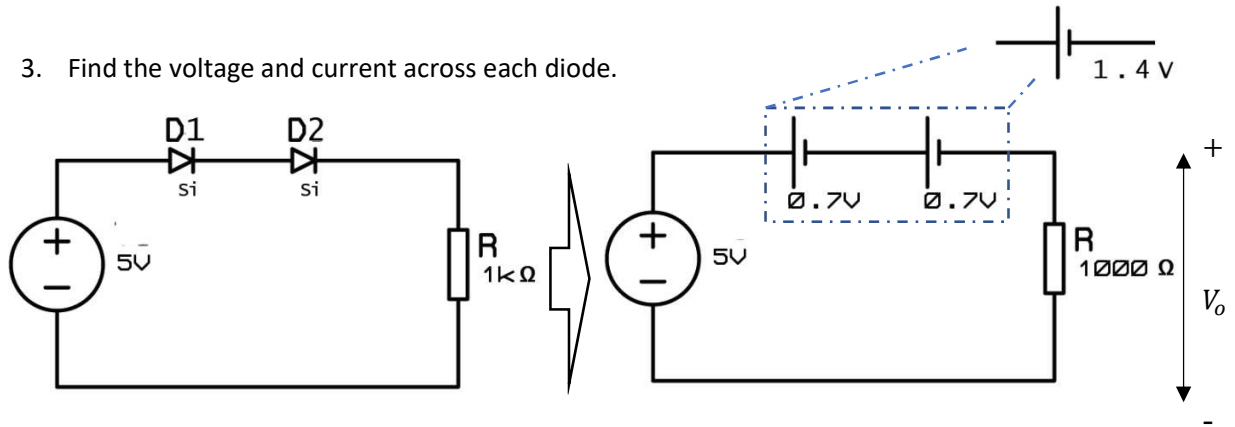3. Find the voltage and current across each diode.




4.

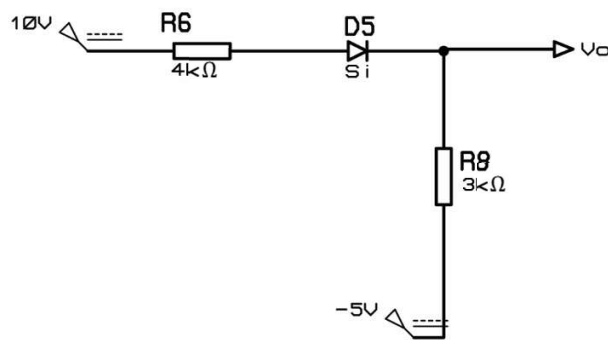

Find V_1 , V_2 and V_D ?

5.

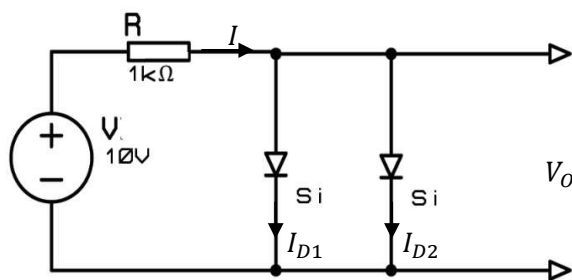

Assume diodes are identical


Find V_D , current I , I_{D1} & I_{D2} for the given circuit.

$$I = I_{D1} + I_{D2}$$



General Sir John Kotelawala Defense University
Basic Electronics
Tutorial 1


6.

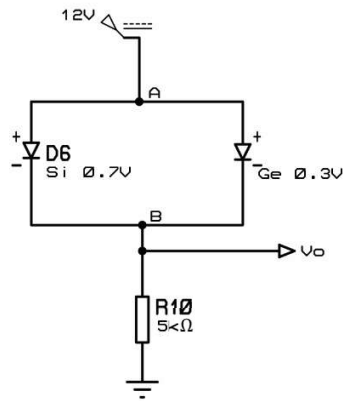

Find the output voltage (V_o) ?

7.

Find output voltage V_o .

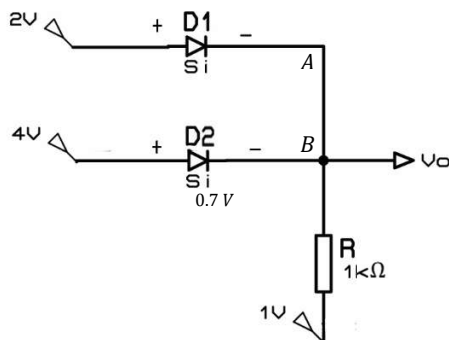

Assume both the diodes are conducting simultaneously.