



GENERAL SIR JOHN KOTELAWALA DEFENCE UNIVERSITY

Faculty of Engineering

Department of Electrical, Electronic and Telecommunication Engineering

B.Sc. Engineering Degree

Semester 6 Examination – September 2022

(Intake 37 - EE/ET/MC)

EE 3213 – POWER ELECTRONICS AND APPLICATIONS I

Time allowed: 3 Hours

23 September 2022

INSTRUCTIONS TO CANDIDATES:

This paper contains 7 questions on 6 pages.

Answer any FIVE Questions only.

This is a closed book examination.

This examination accounts for 70% of the module assessment. The total maximum mark attainable is 100. The marks assigned for each question & sections thereof are indicated in square brackets.

If you have any doubt as to the interpretation of the wording of a question, make your own decision, but clearly state it on the script.

All Examinations are conducted under the rules & regulations of the University

EE 3213

This Page is Intentionally Left Blank

Question 1

- a) ✓ A single-phase full-bridge diode converter is operating on 50 Hz, 230 V single phase AC supply. The converter output feeds a $80\ \Omega$ resistive load. Assume diodes and the AC supply to be ideal. Determine,

- (i) Mean value of load voltage. [02]
- (ii) Peak to peak ripple in output voltage. [02]
- (iii) Peak current through a diode. [02]

- b) ✓ Converter in (a) above is then modified by connecting a $1000\ \mu\text{F}$ capacitor in parallel with the converter output. Determine the new values of,

- (i) Mean load voltage. [04]
- (ii) Peak to peak ripple in output voltage. [04]
- (iii) Peak current through a diode. [04]

Comment on the results in (a) and (b). [02]

Question 2

- a) ✓ Three-phase, full-bridge AC to DC diode-converter is operating on 400 V, 50 Hz three-phase AC supply. The converter delivers 25 A constant current to an inductive load. You may ignore the internal impedance of the AC supply. Assume ideal diodes. Determine,

- (i) Mean value of the output DC voltage. [02]
- (ii) Peak to peak ripple in output voltage. [02]
- (ii) RMS value of the fundamental component of AC side line-current. [02]
- (iii) RMS value and frequency of the lowest order harmonic in AC side line current. [04]

- b) Three-phase, dual-series-bridge AC to DC diode-converter is powered by 400V, 50 Hz, three-phase AC supply via a Dd0v1 three-phase transformer of line-voltage ratio 2:1:1, so that the input voltages to the two bridges have a 30° phase shift. The converter system delivers 25 A constant current to an inductive load. You may ignore the internal impedance of the AC supply and the transformer. Assume ideal diodes. Determine,

- (i) Mean value of the output DC voltage. [02]
- (ii) Peak to peak ripple in output voltage. [02]
- (ii) RMS value of the fundamental component of AC side line-current. [02]
- (iii) RMS value and frequency of the lowest order harmonic in AC side line current. [04]

Question 3

- a) A three phase, full-bridge AC to DC thyristor-converter is operating on 400 V, 50 Hz, three phase AC supply. The converter delivers 6 kW of power to an inductive load at 420 V DC (mean). Supply side inductance is 2 mH per phase. You may assume that the output current is constant and ripple free. Calculate,

- (i) Delay (firing) angle for thyristors. [04]
- (ii) Conduction overlap angle. [04]
- (iii) RMS value of the fundamental component of input line current. [04]

- b) For the converter in (a) above, sketch the following waveforms indicating appropriate values.

- (i) Output voltage. [03]
- (ii) Line-line voltage at the converter input (PCC) showing deep and shallow notches. [03]

Describe briefly how the depths of voltage notches at the PCC in (ii) above are modified in practice to comply with utility standards. [02]

Question 4

- a) Single-phase voltage source inverter is operated with sinusoidal unipolar-PWM control, with carrier-ratio 48, depth of modulation 0.8 and reference frequency 50 Hz. Input DC voltage to the inverter is 420 V. Determine,

- (i) RMS value of the fundamental component of output voltage. [03]
- (ii) Lowest order of significant harmonics in the output voltage [02]
- (iii) Switching frequency of inverter. [02]

Why do we often prefer unipolar PWM over bipolar PWM in practice? [03]

- b) Three-phase, voltage source inverter is operated with Regular sampled PWM control, with carrier-ratio 49, depth of modulation 0.8 and reference frequency 50 Hz. Sinusoidal reference signal is sampled at successive positive peaks of the triangular carrier. Positive-going zero-crossing of the reference signal is taken at a quarter sampling interval after the 0th sampling instant. Calculate the timing of switching signals S_a , S_b & S_c over the 18th sampling-period. [10]

Question 5

- a) Three-phase voltage source inverter is operated with square-wave (six-step) control. Take DC input-voltage as V_d . Give the following waveforms corresponding to balanced three-phase operation.
- (i) Switching signals S_a , S_b & S_c for the legs A , B & C of the inverter. [04]
 - (ii) Phase voltage output. [04]
- b) The output of the inverter in (a) above is connected to a balanced, three-phase, star-connected load with each phase having $20\ \Omega$ resistance in series with 40 mH inductance. Input DC voltage is 420 V and switching cycle time is 24 ms .
- (i) Calculate and sketch the waveform of load current in phase- a . [08]
 - (ii) Sketch the waveform of input current at the DC supply, giving values. [04]

Question 6

- a) A single-phase VSI with input DC voltage V_d is delivering an output current $I_m \sin(\omega t)$ to an inductive load using hysteresis current control with hysteresis band ΔH .
- (i) Give the waveform of output current, indicating running ripple and the tolerance band. [05]
 - (ii) Why the carrier-assisted current control is considered better over the hysteresis current control in practice? [03]
- b) Three-phase voltage source inverter is operated with Square Wave PWM with carrier ratio 9 and depth of modulation 0.7. Input DC voltage is 600 V . Synchronization between square-wave reference signals and triangular carrier signal is done in such a way that the positive-going rising-edge of the square-wave coincides the negative-going zero-crossing of the carrier.
- (i) Construct the line-line voltage waveform at the output. [05]
 - (ii) Determine the magnitude and angular-width in degrees for ON and OFF states of voltage pulses in the waveform in (i) above. [04]
 - (iii) Determine the RMS value of the fundamental component of the line-line voltage. [03]

Question 7

- a) Define the term Voltage Utilization for a PWM voltage source inverter. [02]
Determine the value of Voltage Utilization for a three-phase sinusoidal PWM inverter. [04]
- b) How the Voltage utilization is improved when a third-harmonic signal component is added to sinusoidal three-phase reference signals in a sinusoidal three-phase inverter? [03]
Why this third-harmonic is not re-appeared at the output voltage? [03]
- c) Give a circuit that can be used to modify sinusoidal three-phase reference signals appropriately, in order to increase Voltage utilization without over-modulation for a sinusoidal three-phase inverter. [04]
- d) Explain briefly why it is necessary to increase the carrier-ratio when delivering low-frequency output voltage by a PWM voltage source inverter operated with constant V to f control. [04]

End of Question Paper