

# **Designing MIPS Processor (Single-Cycle)**








# Introduction

- Implementation of the system that includes MIPS processor and memory
- The design will include support for execution of only:
  - memory-reference instructions: **lw & sw**
  - arithmetic-logical instructions: **add, sub, and, or...**
  - control flow instructions: **beq & j**
- But that design will provide us with principles, so many more instructions could be easily added such as: **addu, lb, lbu, lui, addi, adiu, sltu, slti, andi, ori, xor, xori, jal, jr, jalr, bne, beqz, bgtz, bltz, nop, mfhi, mflo, mfe pc, mfco, lwc1, swc1, etc.**


# Single Cycle Design

- first design a simpler processor that executes each instruction in only **one clock cycle time**.
- **This is not efficient from performance point of view**, since:
  - a clock cycle time (i.e. clock rate) must be chosen such that the longest instruction can be executed in one clock cycle and
  - that makes shorter instructions execute in one unnecessarily long cycle.
- Additionally, no resource in the design may be used more than once per instruction, **thus some resources will be duplicated**.
- The single cycle design will require:
  - two memories (instruction and data),
  - two additional adders.

# Elements for Datapath Design

       

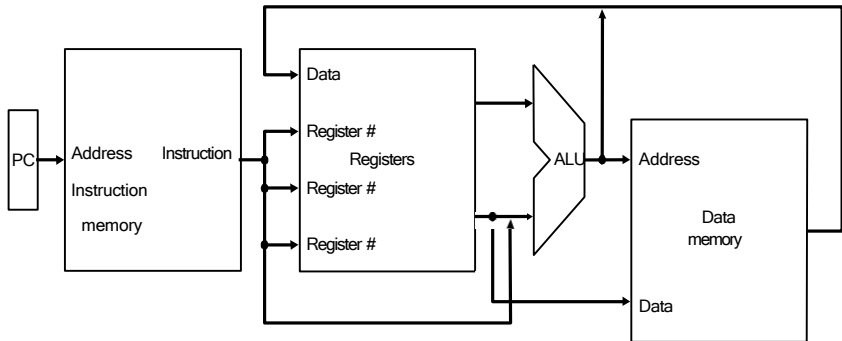
# Abstract /Simplified View (1<sup>st</sup> look)



- This generic implementation:
  - uses the program counter (PC) to supply instruction address,
  - gets the instruction from memory,
  - reads registers,
  - uses the instruction opcode to decide exactly what to do.

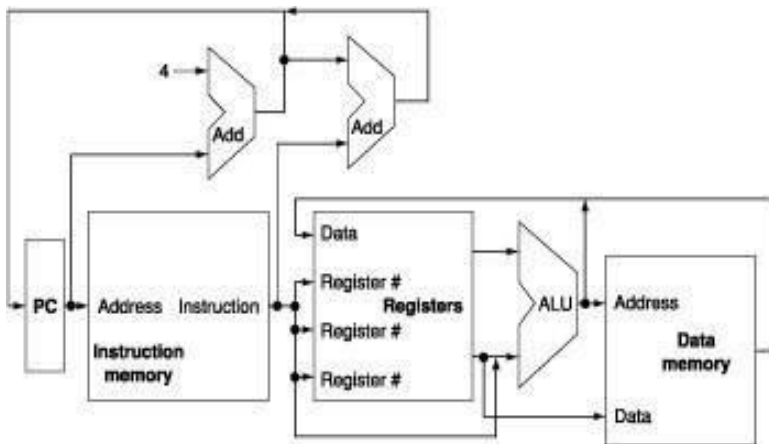
## Abstract /Simplified View (2<sup>nd</sup> look)



- PC is incremented by 4 by most instructions, and  $4 + 4 \times \text{offset}$  by branch instructions.
- Jump instructions change PC differently (not shown)

 
# Our Implementation

- An edge triggered methodology
- Typical execution:
  - read contents of some state elements at the beginning of the clock cycle,
  - send values through some combinational logic,
  - write results to one or more state elements at the **end** of the clock cycle.




- An edge triggered methodology allows a state element to be read and written in the same clock cycle.

# Incrementing PC & Fetching Instruction

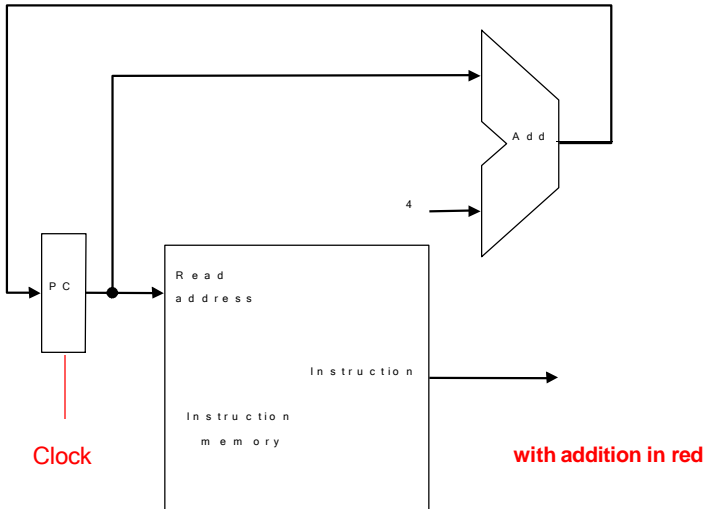




# Datapath for R-type Instructions

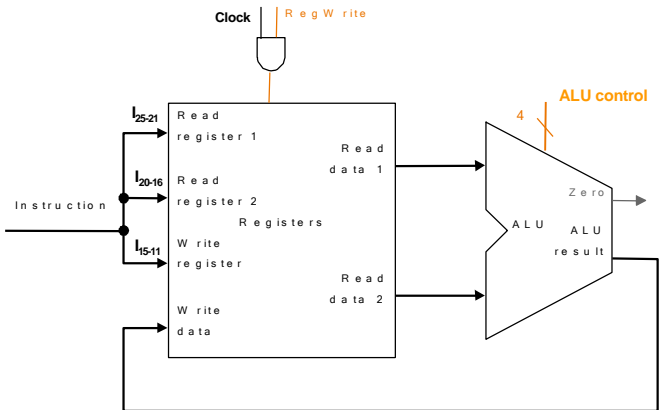


R-type

 


add = 32  
 sub = 34  
 slt = 42  
 and = 36  
 or = 37  
 nor = 39
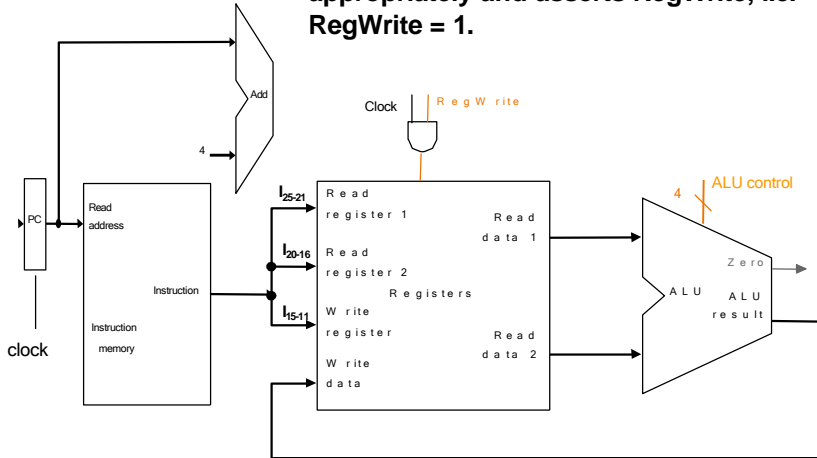
# Complete Datapath for R-type Instructions

Based on contents of op-code and funct fields, Control Unit sets ALU control appropriately and asserts RegWrite, i.e.  $\text{RegWrite} = 1$ .




# Datapath for LW and SW Instructions

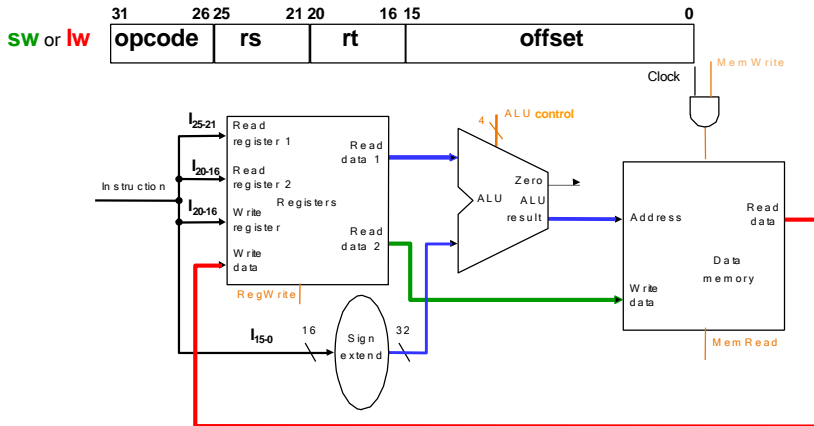

## Control Unit sets:


- ALU control = 0010 (add) for address calculation for both lw and sw
- **MemRead=0, MemWrite=1 and RegWrite=0** for **sw**
- **MemRead=1, MemWrite=0 and RegWrite=1** for **lw**
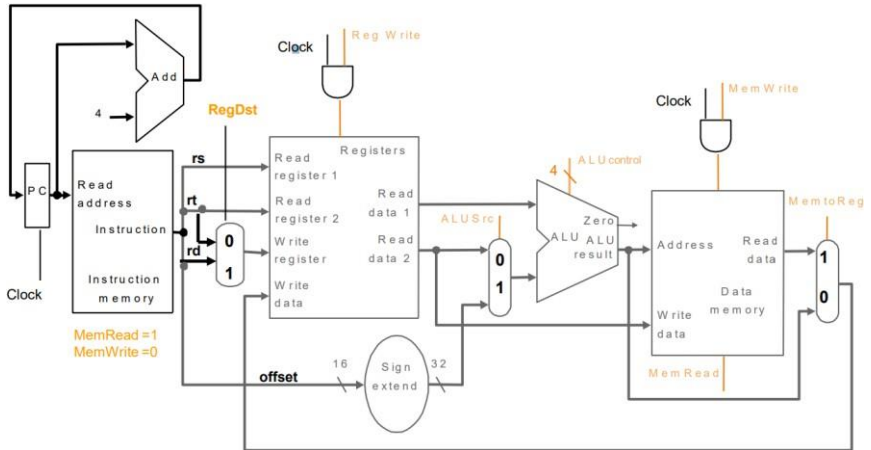
# Datapath for R-type, LW & SW Instructions




Let us determine setting of control lines for R-type, lw & sw instructions.


# Datapath for BEQ Instruction

 


Branch target = [PC] + 4 + 4×offset

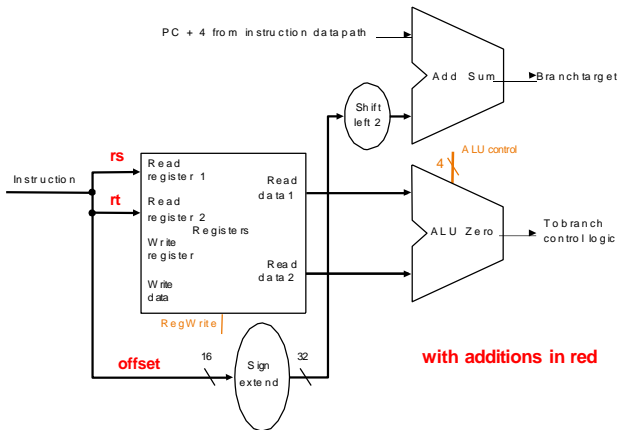

# Datapath for R-type, LW, SW & BEQ

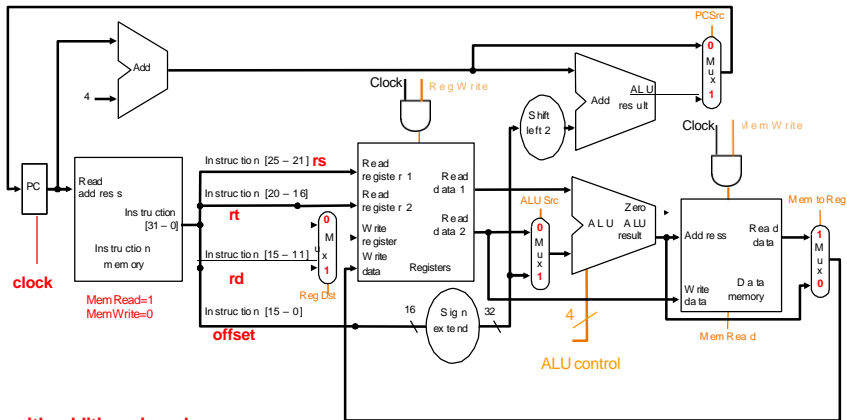

# Control Unit and Datapath

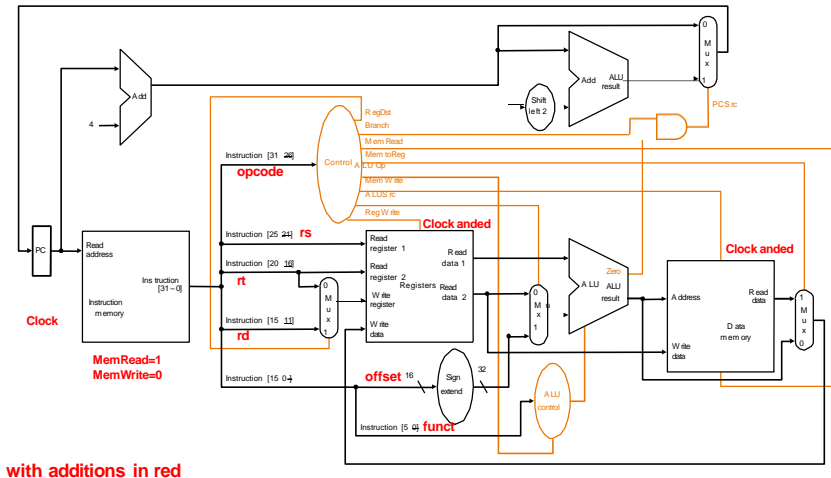

# Truth Table for (Main) Control Unit

	Input			Output						
	Op-code	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUp0
R-type	000000	1	0	0	1	d	0	0	1	0
lw	100011	0	1	1	1	1	0	0	0	0
sw	101011	d	1	d	0	0	1	0	0	0
beq	000100	d	0	d	0	d	0	1	0	1

- **ALUOp[1-0] = 00** → signal to ALU Control unit for ALU to perform add function, i.e. set Ainvert = 0, Binvert=0 and Operation=10
- **ALUOp[1-0] = 01** → signal to ALU Control unit for ALU to perform subtract function, i.e. set Ainvert = 0, Binvert=1 and Operation=10
- **ALUOp[1-0] = 10** → signal to ALU Control unit to look at bits  $I_{[5-0]}$  and based on its pattern to set Ainvert, Binvert and Operation so that ALU performs appropriate function, i.e. add, sub, slt, and, or & nor



# Truth Table of ALU Control Unit

Input								Output
ALUOp		Funct field						ALU Control
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	Control
0	0	d	d	d	d	d	d	0 0 10
0	1	d	d	d	d	d	d	0 1 10
1	0	1	0	0	0	0	0	0 0 10
1	0	1	0	0	0	1	0	0 1 10
1	0	1	0	0	1	0	0	0 0 00
1	0	1	0	0	1	0	1	0 0 01
1	0	1	0	1	0	1	0	0 1 11
1	0	1	0	0	1	1	1	1 1 00

add  
sub  
add  
sub  
and  
or  
slt  
nor


Ainvert Bivert Operation

# Design of (Main) Control Unit


Op-code bits 5 4 3 2 1 0	RegDst	ALUSrc	MemtoReg	RegWrite	MemRead	MemWrite	Branch	ALUOp1	ALUOp0
0 0 0 0 0 0	1	0	0	1	d	0	0	1	0
1 0 0 0 1 1	0	1	1	1	1	0	0	0	0
1 0 1 0 1 1	d	1	d	0	0	1	0	0	0
0 0 0 1 0 0	d	0	d	0	d	0	1	0	1

$$\text{RegDst} = \overline{\text{Op}_5} \overline{\text{Op}_4} \overline{\text{Op}_3} \overline{\text{Op}_2} \overline{\text{Op}_1} \overline{\text{Op}_0}$$

 
$$\begin{aligned} \text{ALUSrc} = & \overline{\text{Op}_5} \overline{\text{Op}_4} \overline{\text{Op}_3} \overline{\text{Op}_2} \overline{\text{Op}_1} \overline{\text{Op}_0} \\ & + \overline{\text{Op}_5} \overline{\text{Op}_4} \overline{\text{Op}_3} \overline{\text{Op}_2} \text{Op}_1 \text{Op}_0 \end{aligned}$$



# Datapath for R-type, LW, SW, BEQ & J

 
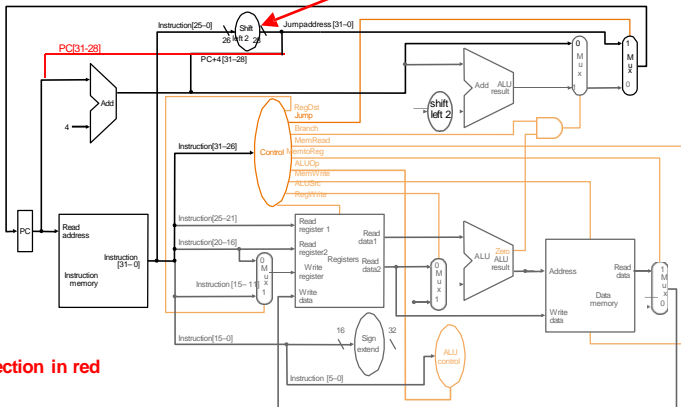
$$PC \leftarrow PC_{31-28} \parallel \text{jump\_target} \parallel 00$$



with correction in red


# Design of Control Unit (J included)

Op-code bits 5 4 3 2 1 0	RegDst	ALUSrc	MemtoReg	RegWrite	MemRead	MemWrite	Branch	ALUOp1	ALUOp0	Jump
0 0 0 0 0 0	1	0	0	1	d	0	0	1	0	0
1 0 0 0 1 1	0	1	1	1	1	0	0	0	0	0
1 0 1 0 1 1	d	1	d	0	0	1	0	0	0	0
0 0 0 1 0 0	d	0	d	0	d	0	1	0	1	0
0 0 0 0 1 0	d	d	d	0	d	0	d	d	d	...1

J

$$\text{Jump} = \overline{\text{Op}_5} \overline{\text{Op}_4} \overline{\text{Op}_3} \overline{\text{Op}_2} \overline{\text{Op}_1} \overline{\text{Op}_0}$$

Inputs

 

No changes in ALU Control unit

# Cycle Time Calculation

- Let us assume that the **only** delays introduced are by the following tasks:
  - Memory access (read and write time = 3 nsec)
  - Register file access (read and write time = 1 nsec)
  - ALU to perform function (= 2 nsec)
- Under those assumption here are instruction execution times:

Instr	fetch		Reg read		ALU oper		Data memory		Reg write	Total
R-type	3	+	1	+	2	+			1	= 7 nsec
lw	3	+	1	+	2	+	3	+	1	= 10 nsec
sw	3	+	1	+	2	+	3			= 9 nsec
branch	3	+	1	+	2					= 6 nsec
jump	3									= 3 nsec

- Thus a clock cycle time has to be 10nsec, and  
clock rate =  $1/10 \text{ nsec} = 100\text{MHz}$

# Single Cycle Processor: Conclusion

- Single Cycle Problems:
  - what if we had a more complicated instruction like floating point?
  - a clock cycle would be much longer,
  - thus for shorter and more often used instructions, such as add & lw, wasteful of time.
- One Solution:
  - use a “smaller” cycle time, and
  - have different instructions take different numbers of cycles.
- And that is a “multi-cycle” processor.