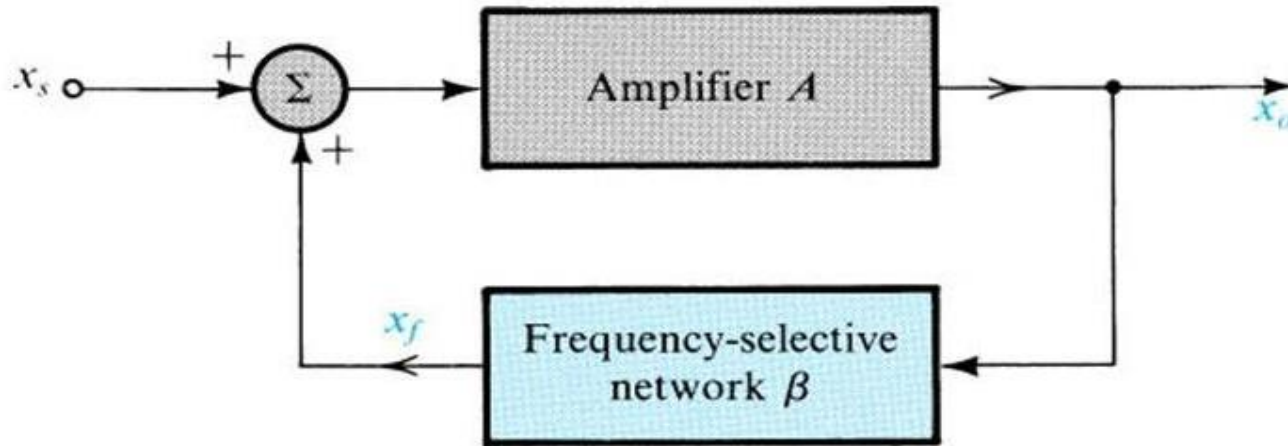


# OSCILLATORS

# OSCILLATORS

- ▶ Employs positive feedback loop consisting of an amplifier and an RC or LC frequency selective circuit.
- ▶ Amplitude of the generated sine wave is limited by using non linear mechanism.

# OSCILLATOR FEEDBACK LOOP



The basic structure of a sinusoidal oscillator.

- A **positive-feedback loop** is formed by an amplifier  $A$  and a frequency-selective network  $\beta$ .
- In an actual oscillator circuit, no input signal will be present; here an input signal  $x_s$  is employed to help explain the principle of operation.

# BASIC PRINCIPLES OF SINUSOIDAL OSCILLATOR

- Nonlinear amplitude control
  - To ensure that oscillations will start, the  $A\beta$  is slightly greater than unity.
  - As the power supply is turned on, oscillation will grow in amplitude.
  - When the amplitude reaches the desired level, the nonlinear network comes into action and cause the  $A\beta$  to exactly unity.



# OSCILLATOR FEEDBACK LOOP

Loop gain  $L(S) = A(S) \cdot \beta(S)$

$$A_f(s) = \frac{A(s)}{1 - A(s) \cdot \beta(s)} = \frac{A(s)}{1 - L(s)}$$

- ▶ If at frequency  $\omega_0$  the loop gain is equal to unity;  $A_f$  will be infinite.
- ▶ That is at that frequency circuit will have a finite output for zero input signal.

# BARKHAUSEN CRITERIA

- ▶ At  $\omega_0$ , the phase of the loop gain should be zero and the magnitude of the loop gain should be unity.
- ▶ That is for the circuit to oscillate at one frequency the oscillation criterion should be satisfied at  $\omega_0$ .

$$x_f = \beta x_0$$

$$Ax_f = x_0$$

$$A\beta x_0 = x_0$$

$$A\beta = 1$$

# BARKHAUSEN CRITERIA

- For the circuit to produce sustained oscillations at a frequency  $\omega_0$  the characteristic equation has to have a roots at  $s = \pm j\omega$ .

Thus  $1 - A(s) \cdot \beta(s)$  should have a factor of the form of

$$s^2 + \omega_0^2$$

# OSCILLATOR CIRCUITS


- Op Amp-RC Oscillator Circuits
  - The Wien-Bridge Oscillator
  - The phase-Shift Oscillator
- LC-Tuned Oscillator
  - Colpitts oscillator
  - Hareley oscillator
- Crystal Oscillator





# RC OSCILLATOR CIRCUIT


- The Wein Bridge Oscillator

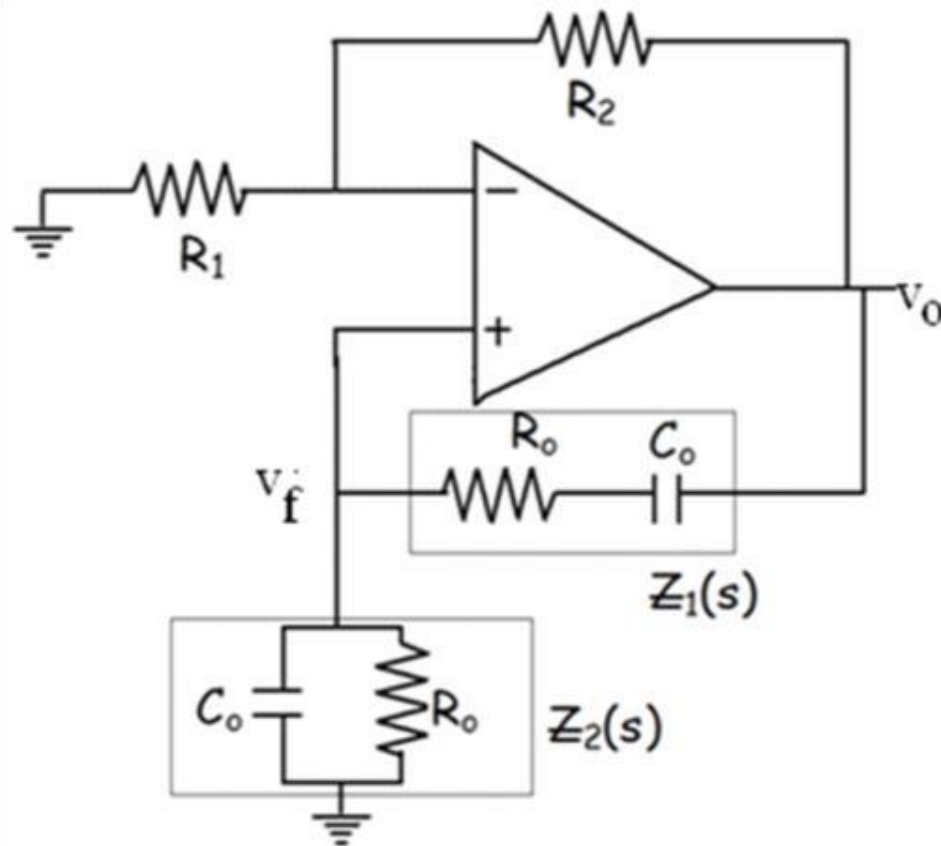

# LC OSCILLATORS

- ▶ Resonance - A condition in a circuit containing inductance and capacitance where the inductive reactance is equal to the capacitive reactance
- ▶ Resonant circuit is also called as LC tank circuit

# BASIC LC OSCILLATOR CIRCUIT

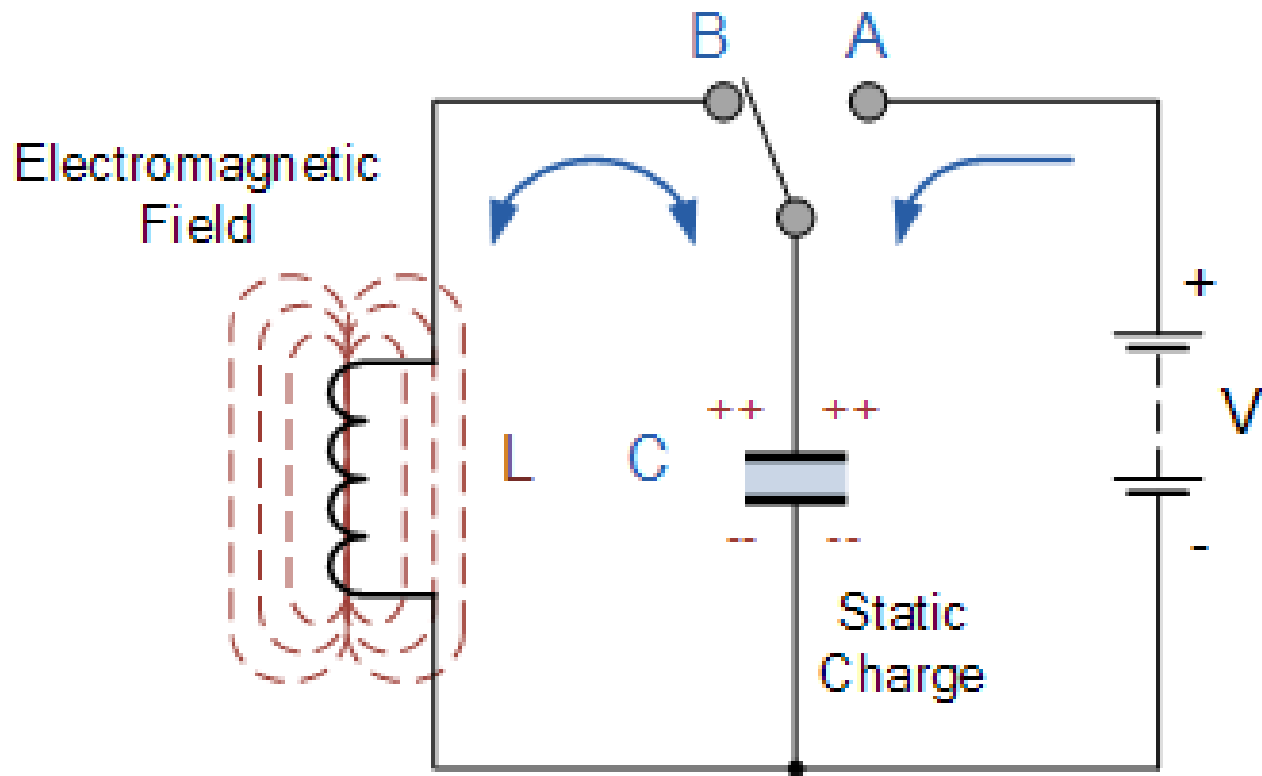


# BASIC LC OSCILLATOR CIRCUIT

- ▶ The capacitor stores energy in the form of an electrostatic field and inductive coil stores its energy in the form of electromagnetic field.
- ▶ The capacitor is charged upto the DC supply voltage,  $V$  by putting the switch position A. When capacitor is fully charged the switch changes to position B.
- ▶ Capacitor begins to discharge itself through coil.
- ▶ The rising current sets up an electromagnetic field around the coil which resists this flow of current.

# BASIC LC OSCILLATOR CIRCUIT

- ▶ When capacitor C is completely discharged the energy stored in the capacitor is now stored in the inductive coil as an electromagnetic field around the coil winding.
- ▶ Then it starts to fall as the electromagnetic field begins to collapse.
- ▶ Back emf  $e = -L \frac{di}{dt}$  keeping the current flowing in the original direction.
- ▶ This current charges up capacitor with opposite polarity.
- ▶ The polarity of the voltage changes as the energy is passed back and forth between the capacitor and the inductor.
- ▶ If there is no loss this will continue indefinitely.

# REACTANCE VS. REACTANCE

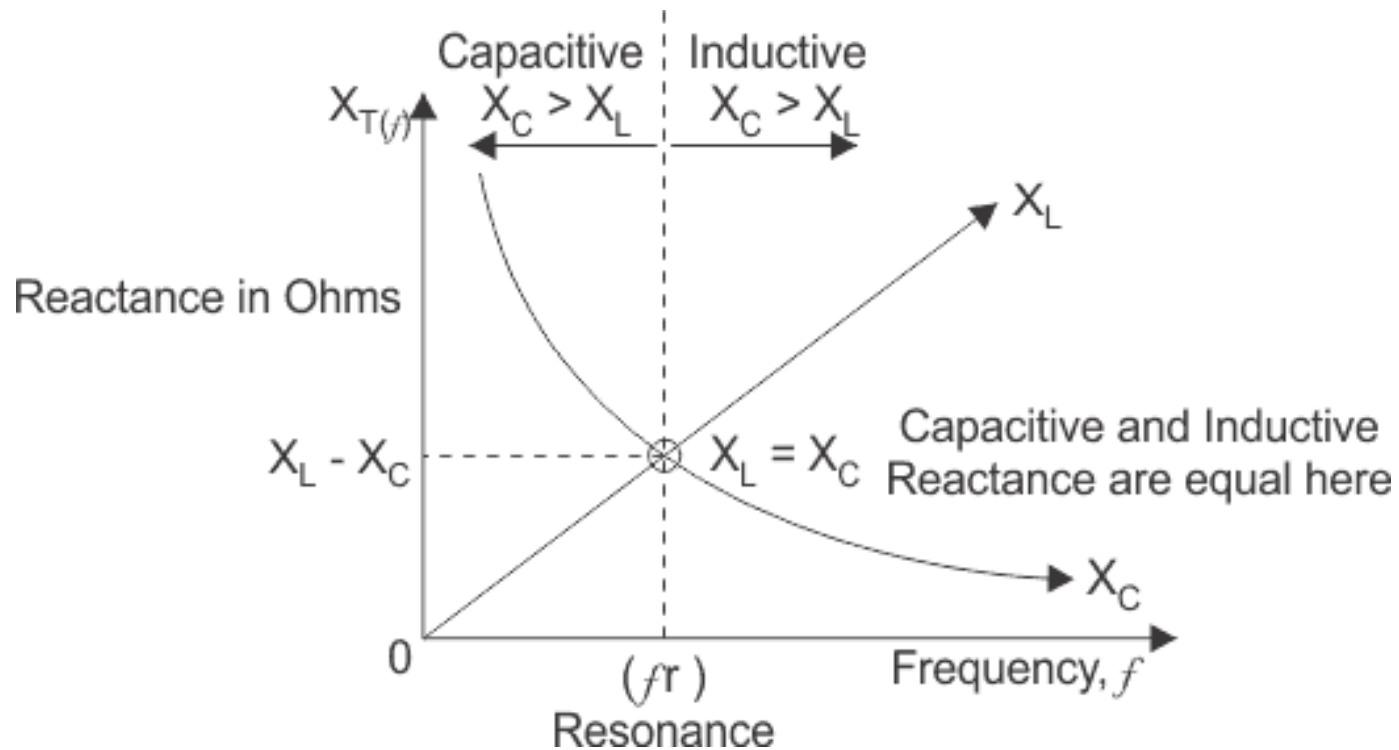


$$X_L = 2\pi fL$$
$$X_C = \frac{1}{2\pi fC}$$

At Resonance  $X_L = X_C$

Therefore  $2\pi fL = \frac{1}{2\pi fC}$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

# THE COLPITTS OSCILLATOR

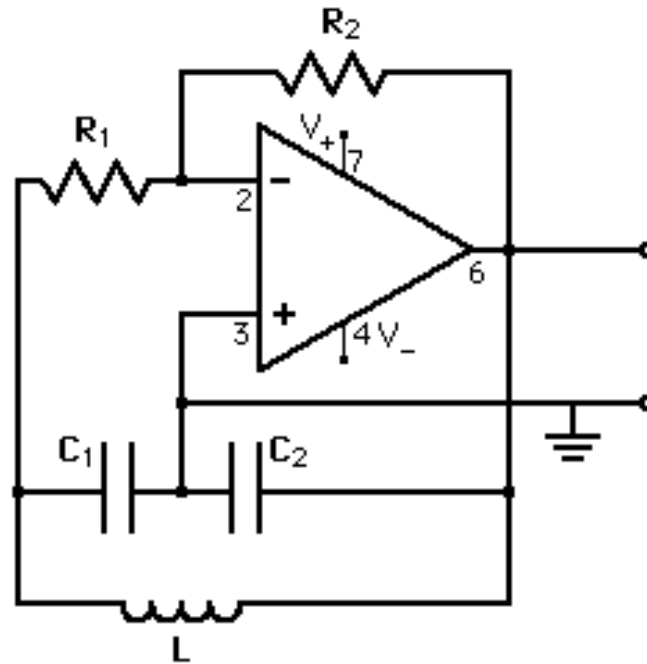


$$f = \frac{1}{2\pi\sqrt{LC}}$$

Where  $C$  is the equivalent value of the capacitance and equal to  $\frac{C_1 C_2}{C_1 + C_2}$

$$f = \frac{1}{2\pi\sqrt{L\left(\frac{C_1 C_2}{C_1 + C_2}\right)}}$$



# THE HARTLEY OSCILLATOR

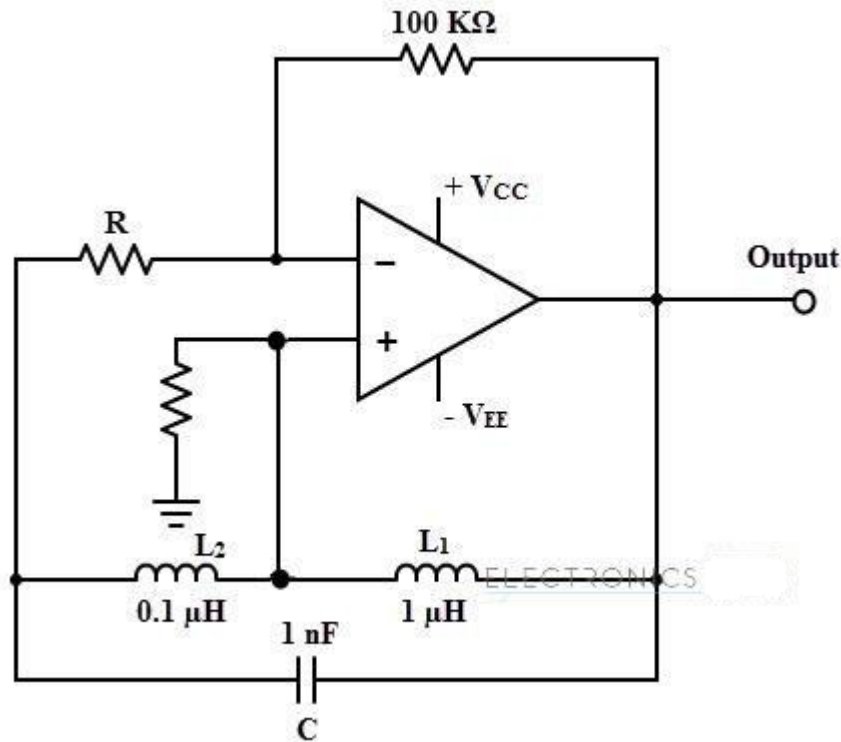

$$f_r = \frac{1}{2\pi\sqrt{L_T C}} = \frac{1}{2\pi\sqrt{(L_1 + L_2) C}}$$

# CRYSTAL OSCILLATORS

- ▶ Frequency stability is affected by variation in temperature, variations in the load and changes in dc power supply.
- ▶ Crystal Oscillator provides frequency stability under these varying conditions.
- ▶ The oscillator frequency is essentially determined by the crystal and not by the rest of the circuit.

# CRYSTAL OSCILLATORS

