

General Sir John Kotelawala Defence University
ET3212 Microwave Engineering
Transmission Lines - Exercises

Upeka Premaratne

Department of Electronic and Telecommunication Engineering
University of Moratuwa

September 21, 2020

Exercise 1

A transmission line has a per unit length inductance of 400 nH/m and per unit length capacitance of 70 pF/m . Calculate the characteristic impedance of the transmission line.

Exercise 2

The per unit length values of inductance, capacitance, resistance and dielectric conductance of a transmission line at 100 MHz are given by 190 nH, 75 pF, 2.6 m Ω and 67 S respectively. Find

- 1 The characteristic impedance
- 2 The propagation coefficient at 100 MHz
- 3 The attenuation of the transmission line in decibels per meter.

Exercise 3

Find the phase velocity of the transmission lines of Exercise 1 and Exercise 2.

Exercise 4

A power amplifier with an output of 200 mW is connected to a $50\ \Omega$ transmission line which is subsequently connected to an antenna with an impedance of $58 + j10\ \Omega$. If the output impedance of the power amplifier is $48\ \Omega$ calculate

- 1 the reflection coefficient between the power amplifier and transmission line
- 2 the reflection coefficient between the transmission line and antenna and
- 3 the power radiated from the antenna.

Exercise 5

The antenna of a low power microwave communication module reflects 6.3% of the power back in to the transmission line.
Calculate the VSWR between the transmission line and antenna.

Exercise 6

An antenna datasheet mentions the maximum VSWR as 1.5 dB. Find the maximum possible value of the reflection coefficient ρ_0 .

Exercise 7

A coaxial microwave transmission line operates at a frequency of 2.4 GHz. It has core and shielding radii of 0.5 mm and 2.3 mm respectively. It has a characteristic impedance of $50\ \Omega$.

- 1 Find the required relative permittivity (ϵ_r) of the dielectric medium of the coaxial cable.
- 2 Calculate the per unit length inductance and capacitance of the coaxial cable.
- 3 Verify the feasibility of the cable parameters.

Exercise 8

The substrate of a printed circuit board has a relative permittivity (ϵ_r) of 4.2 and thickness of 1.5 mm. The one sided copper layer has a thickness of 0.5 mm. Find the characteristic impedance of a slotline with a width of 1 mm and spacing of 2.5 mm.

Exercise 9

A printed circuit board has a relative permittivity (ϵ_r) of 4.3 and thickness of 1.4 mm which excludes the 0.6 mm copper layer on either side. Calculate the characteristic impedance of the resulting microstrip transmission line if the width is

- 1 a narrow 0.8 mm
- 2 a wide 3.4 mm

Exercise 10

The printed circuit board of a microwave circuit has a thickness (h) of 2.5 mm, copper thickness (t) of 0.7 mm and relative permittivity (ϵ_r) of 4.2. The circuit requires a microstrip transmission line to connect a power amplifier output to a printed antenna. The required impedance of the transmission line is $170\ \Omega$. Using a suitable approximation find the required width (w) of the microstrip.